

## Lab Assignment - 4

Name: RAKSAN BASHAR

ID : 17301042

Section: 12

Course: CSE350

# Circuit-1

20-17301042

| Input configuration | D | C | B | A | Output $V_o$ (V) |
|---------------------|---|---|---|---|------------------|
| 1                   | 0 | 0 | 0 | 0 | 0.0027           |
| 2                   | 0 | 0 | 0 | 5 | -0.497           |
| 3                   | 0 | 0 | 5 | 0 | -0.997           |
| 4                   | 0 | 0 | 5 | 5 | -1.497           |
| 5                   | 0 | 5 | 0 | 0 | -1.997           |
| 6                   | 0 | 5 | 0 | 5 | -2.497           |
| 7                   | 0 | 5 | 5 | 0 | -2.997           |
| 8                   | 0 | 5 | 5 | 5 | -3.497           |
| 9                   | 5 | 0 | 0 | 0 | -3.997           |
| 10                  | 5 | 0 | 0 | 5 | -4.497           |
| 11                  | 5 | 0 | 5 | 0 | -4.997           |
| 12                  | 5 | 0 | 5 | 5 | -5.497           |
| 13                  | 5 | 5 | 0 | 0 | -5.997           |
| 14                  | 5 | 5 | 0 | 5 | -6.497           |
| 15                  | 5 | 5 | 5 | 0 | -6.997           |
| 16                  | 5 | 5 | 5 | 5 | -7.497           |

2

Id-173010

circuit-2

| input configuration | D | C | B | A | Output $V_o(V)$ |
|---------------------|---|---|---|---|-----------------|
| 1                   | 0 | 0 | 0 | 0 | .0049           |
| 2                   | 0 | 0 | 0 | 5 | -0.620          |
| 3                   | 0 | 0 | 5 | 0 | -1.245          |
| 4                   | 0 | 0 | 5 | 5 | -1.869          |
| 5                   | 0 | 5 | 0 | 0 | -2.495          |
| 6                   | 0 | 5 | 0 | 5 | -3.119          |
| 7                   | 0 | 5 | 5 | 0 | -3.744          |
| 8                   | 0 | 5 | 5 | 5 | -4.369          |
| 9                   | 5 | 0 | 0 | 0 | -4.994          |
| 10                  | 5 | 0 | 0 | 5 | -5.619          |
| 11                  | 5 | 0 | 5 | 0 | -6.244          |
| 12                  | 5 | 0 | 5 | 5 | -6.869          |
| 13                  | 5 | 5 | 0 | 0 | -7.494          |
| 14                  | 5 | 5 | 0 | 5 | -8.119          |
| 15                  | 5 | 5 | 5 | 0 | -8.744          |
| 16                  | 5 | 5 | 5 | 5 | -9.369          |






3

106-17301042

(1).



Let's take  $\alpha = 0.0015$ .Here,  $A = 10V$  $B, C, D = 0V$ .

Now, By applying source transformation.

     

22


(P.V.D)

  


$$\begin{aligned}
 \therefore V_1 &= \frac{20}{20+20} \times 0.62 \\
 &= \frac{20}{40} \times 0.62 \\
 &= 0.3125
 \end{aligned}$$

~ Again,
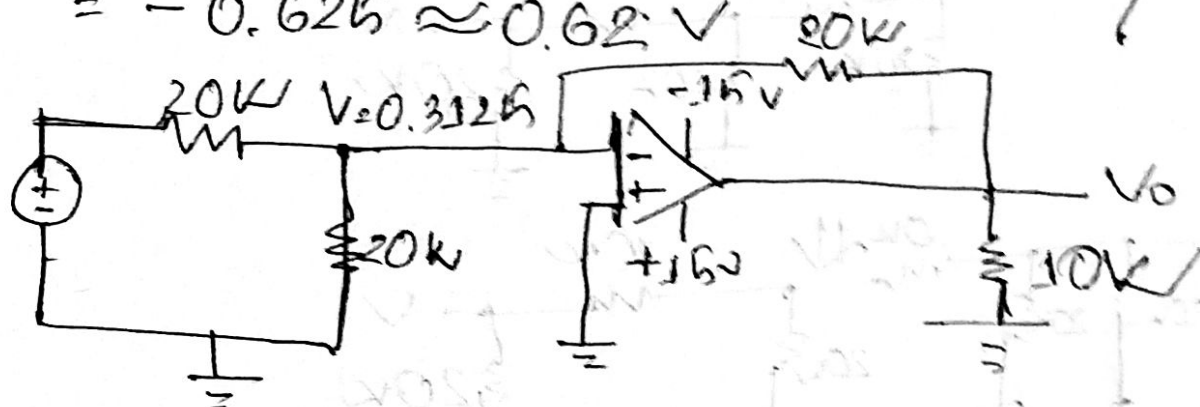
$$\begin{aligned}
 V_0 &= - \left\{ \left( \frac{20}{20} \times 0.62 \right) + \frac{20}{20} \times 0 \right\} \\
 &= -0.625 \approx -0.62 \text{ V}
 \end{aligned}$$



 From previous circuit 2, we get  $-0.620 \text{ V}$  for the input (0003) and through calculation we get  $-0.625$ . These are basically the same.



(2)

The last two digits are 4 and 2.  
 $\therefore \text{VO high} = 6, \text{ low} = 0.$

| input configurations | D | C | B | A | output |
|----------------------|---|---|---|---|--------|
| 1                    | 0 | 0 | 0 | 0 | 0.0027 |
| 2                    | 0 | 0 | 0 | 6 | -0.597 |
| 3                    | 0 | 0 | 6 | 0 | -1.197 |
| 4                    | 0 | 0 | 6 | 6 | -1.797 |
| 5                    | 0 | 6 | 0 | 0 | -2.397 |
| 6                    | 0 | 6 | 0 | 6 | -2.997 |
| 7                    | 0 | 6 | 6 | 0 | -3.597 |
| 8                    | 0 | 6 | 6 | 6 | -4.197 |
| 9                    | 6 | 0 | 0 | 0 | -4.497 |
| 10                   | 6 | 0 | 0 | 6 | -5.097 |
| 11                   | 6 | 0 | 6 | 0 | -5.697 |
| 12                   | 6 | 0 | 6 | 6 | -6.297 |
| 13                   | 6 | 6 | 0 | 0 | -6.897 |
| 14                   | 6 | 6 | 0 | 6 | -7.497 |
| 15                   | 6 | 6 | 6 | 0 | -8.097 |
| 16                   | 6 | 6 | 6 | 6 | -8.697 |

(P.V.O)



(3)

For both the converters -  
Here, input is 4 bits.

$$\therefore \text{full step output} = 2^4 - 1 \\ = 15 \text{ steps}$$

Binary weighted resistors

$$\text{step size} = -0.497$$

$$\text{full scale} = -7.497$$

$\therefore$  resolution

$$\therefore \text{resolution} = \frac{-0.497}{-0.749 - 7.497} \\ = 0.0662$$

R and 2R

$$\text{step size} = -0.620$$

$$\text{full scale} = -9.369$$

$$\therefore \text{resolution} = \frac{-0.620}{-9.369} = 0.0661$$

(4)

The step size corresponds to the RF.

if we increase RA step size will also increase proportionately.

Similarly, decreasing the value of RA will also decrease step size proportionately.


7

ID-17301042

 (5)

In the above D2A converters  
the bias voltages are  $-15V$  and  
 $+15V$ .

So it is not possible to get  
an output lower than  $-15V$  unless  
these bias voltages are changed.




(P.V.D)




8

# circuit-1 (Binary weighted-resistor)

 


# 9 circuit-2 (R-2R)

Id-17301042

 




Schematic Capture X

 

P L DEVICES

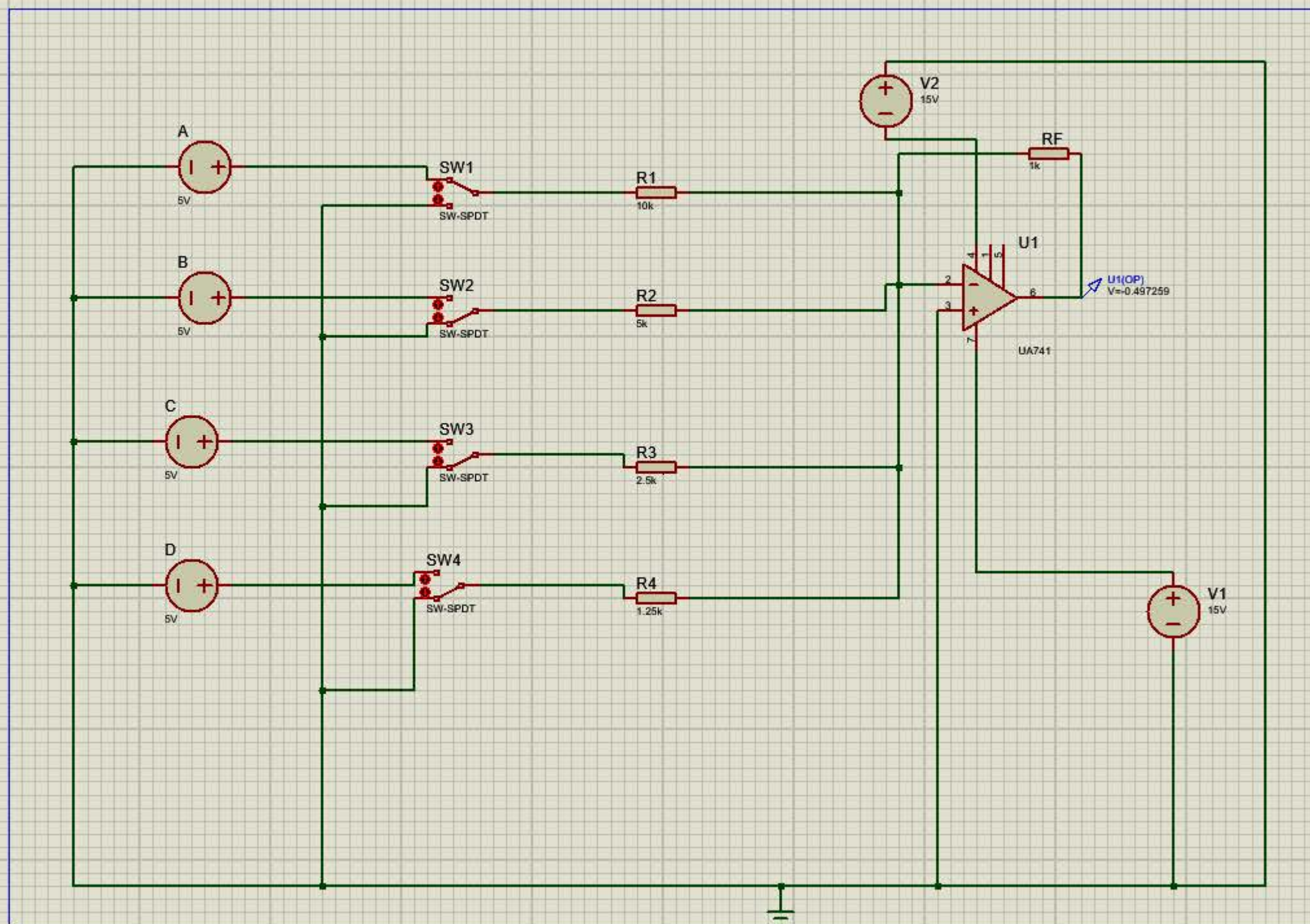RES  
SW-SPDT  
UA741  
VSOURCE





Schematic Capture X

