




Signal Generators

LECTURE 16

This document might contain some excerpts and pictures from various books and other sources. The author doesn't claim any rights to the topics discussed in this video. This topics has been presented in a way to help out students in BRAC university, Bangladesh

Basic RC circuit

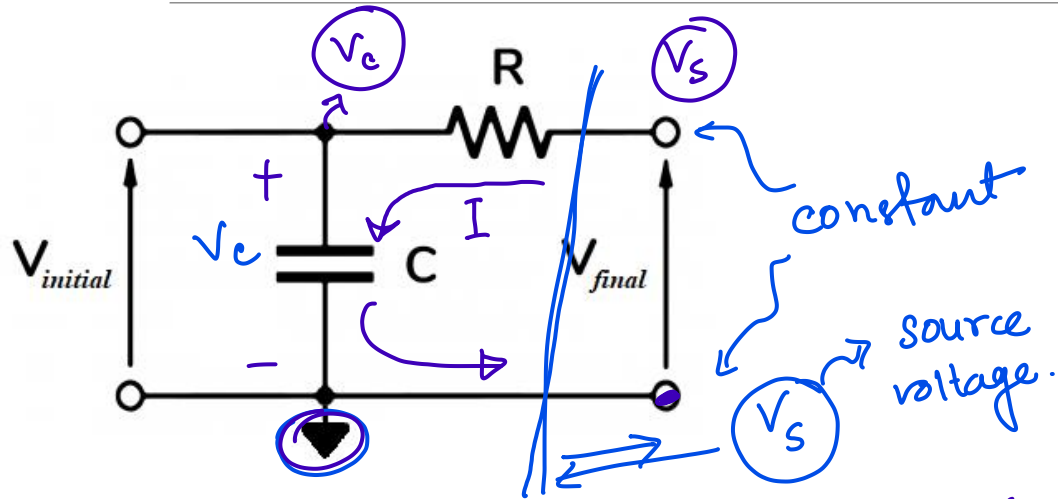

$$C \equiv \frac{Q}{V_c}$$

$$t_1 < t_2 < \infty$$

$$\int_{V_c(t_1)}^{V_c(t_2)} \frac{dV_c}{V_s - V_c} = \frac{1}{RC} \int_{t_1}^{t_2} dt \Rightarrow$$

$t = t_1$, rest of the circuit is connected to RC circuit, $V_c(t = t_1) = V_{\text{initial}}$

$V_c < V_s$. $Q \uparrow$, $V_s < V_c$. $Q \downarrow$.

$$I = \frac{dQ}{dt} = \frac{d(CV)}{dt} = C \frac{dV_c}{dt}$$

$$I = \frac{V_s - V_c}{R} \therefore \boxed{C \frac{dV_c}{dt} = \frac{V_s - V_c}{R}} \Rightarrow \frac{dV_c}{V_s - V_c} = \frac{dt}{RC}$$

$\tau = RC = \text{time constant}$

$$-\ln \left| \frac{V_s - V_c(t_2)}{V_s - V_c(t_1)} \right| = \frac{1}{RC} (t_2 - t_1) \Rightarrow (t_2 - t_1) = RC \ln \left| \frac{V_s - V_c(t_1)}{V_s - V_c(t_2)} \right|$$



$$\Rightarrow V_c(t_2) = V_s + (V_c(t_1) - V_s) e^{-\frac{(t_2 - t_1)}{\tau}}$$

Astable Multivibrator

$$V_c(t_1) = \text{initial voltage.}$$

$$t_2 \rightarrow \infty, e^{-(t_2-t_1)/\tau} = e^{-\infty} \rightarrow 0$$

$$V_c(t_2 \rightarrow \infty) = V_s$$

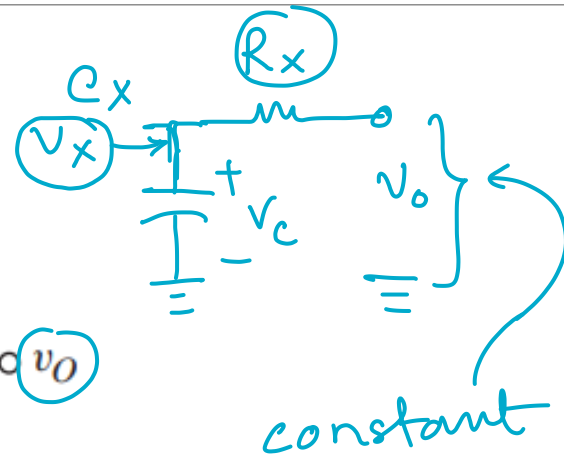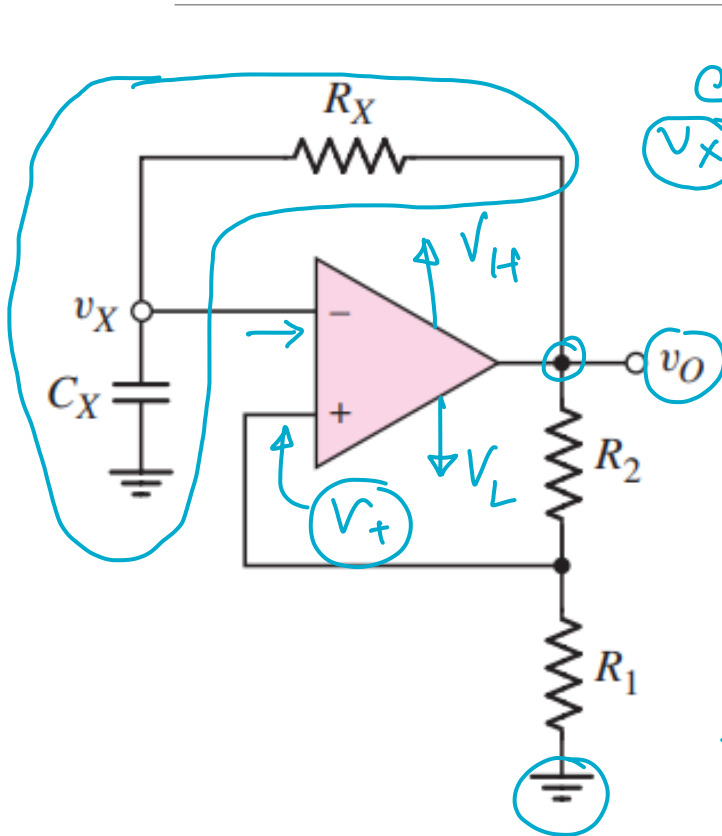

$$v_X = v_O + (v_{\text{initial}} - v_O) e^{-\frac{(t_2-t_1)}{\tau}}$$

$\tau = R_X C_X$


$v_s = v_{\text{final}}$

$$t_2 - t_1 = \tau \ln \left| \frac{V_{\text{final}} - V_c(t_1)}{V_{\text{final}} - V_c(t_2)} \right|$$

Neamom $\rightarrow V_{TH} = V_H \left(\frac{R_1}{R_1 + R_2} \right), V_{TL} = V_L \left(\frac{R_1}{R_1 + R_2} \right)$

Coughline chapter 6

Square Wave Generator

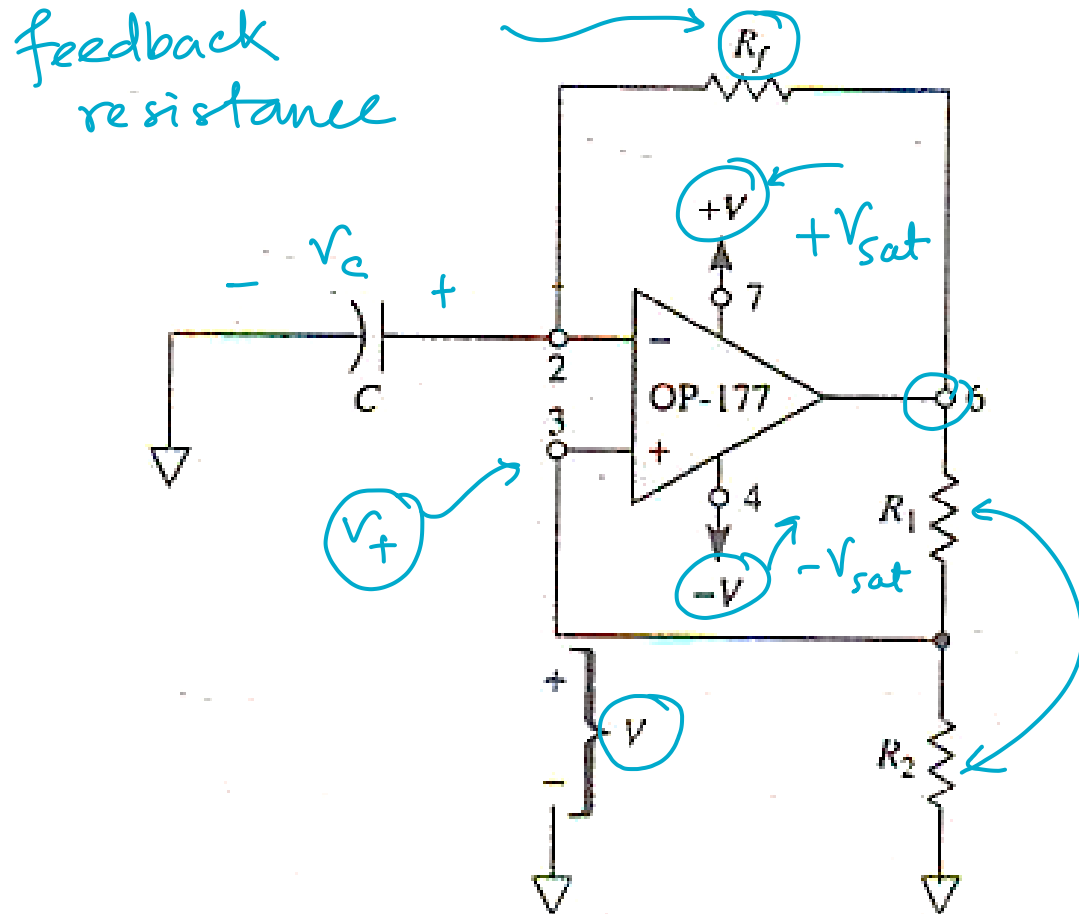

➤ V_{UT} is given in equation

$$V_{UT} = \frac{R_2}{R_1 + R_2} (+V_{sat})$$

V_H

upper threshold

➤ V_{LT} is given in equation



$$V_{LT} = \frac{R_2}{R_1 + R_2} (-V_{sat})$$

V_L

lower threshold

Square Wave Generator

Steady State Behavior

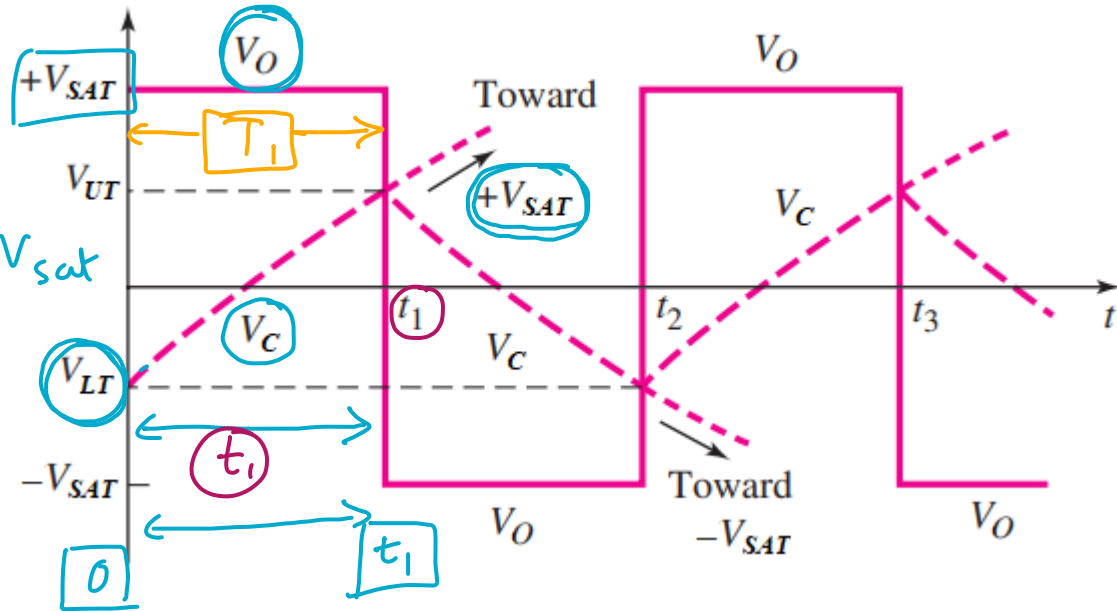
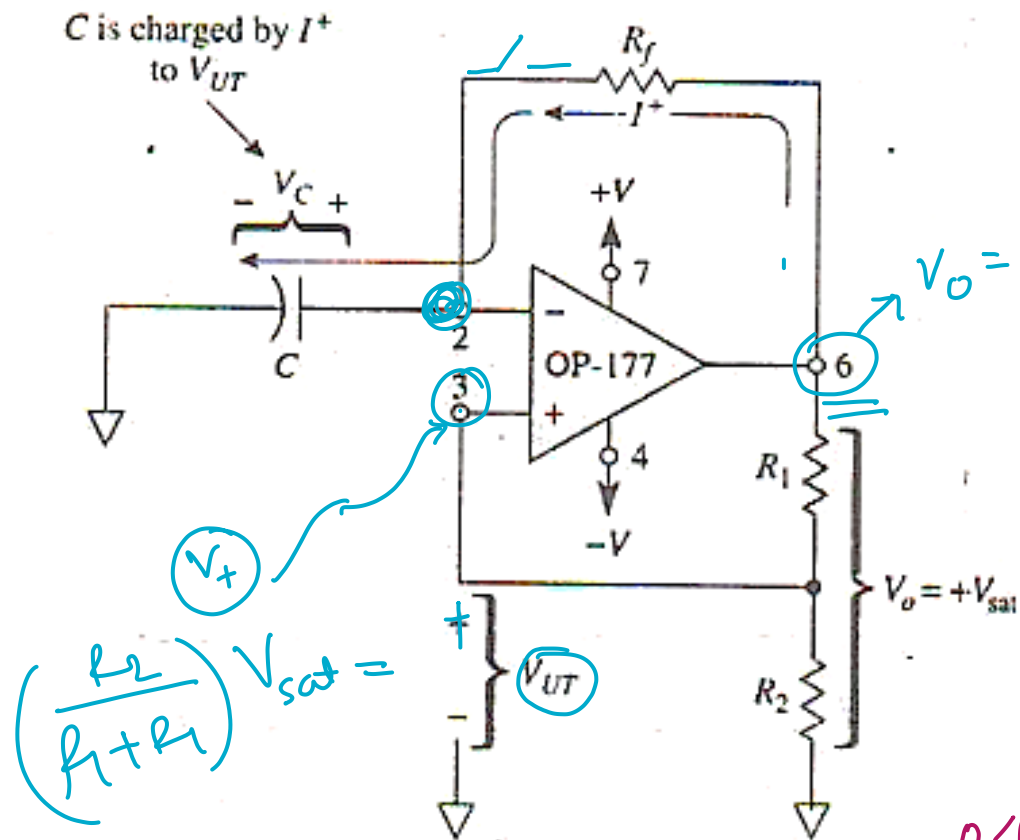


$$V_{LT} = \left(\frac{R_2}{R_1 + R_2}\right) (-V_{sat})$$

$$0 < t < t_1, \quad V_C(t) = V_{sat} + (V_{LT} - V_{sat}) e^{-\left(\frac{t-0}{R_f C}\right)}$$

$$V_C(t_1) = V_{UT} \quad T_1 = t_1 = R_f C \ln \left(\frac{V_{sat} - V_{LT}}{V_{sat} - V_{UT}} \right) \checkmark$$


Square Wave Generator

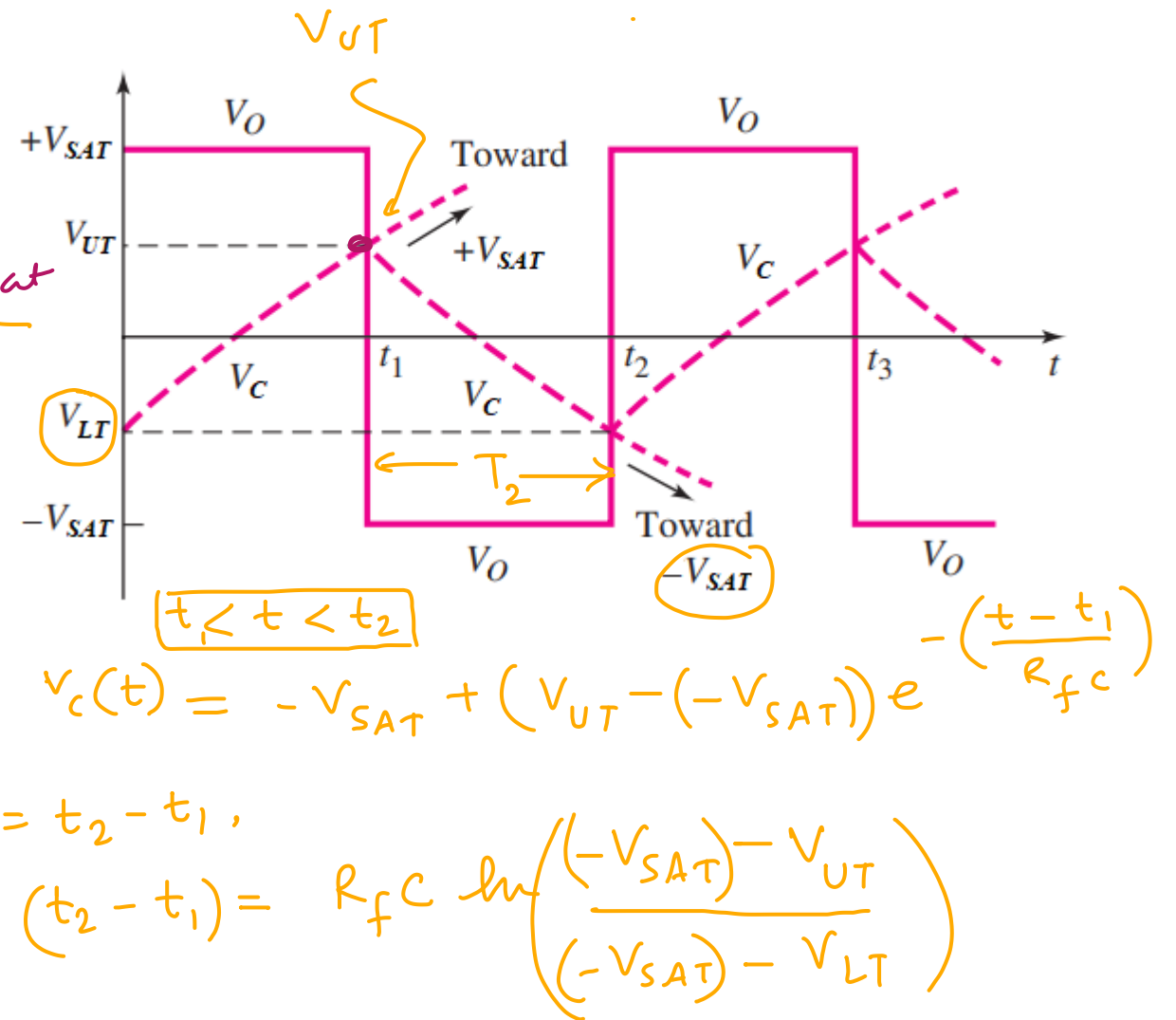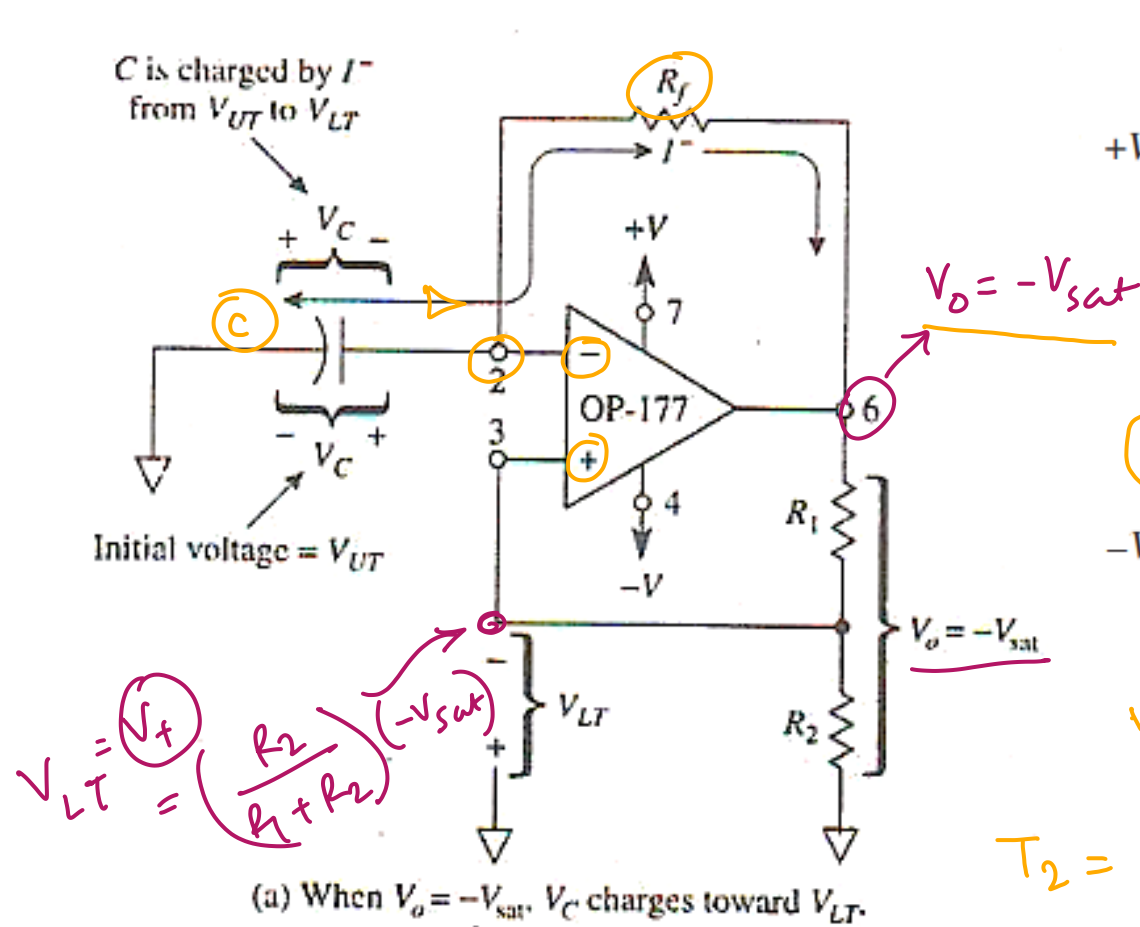


Square Wave Generator

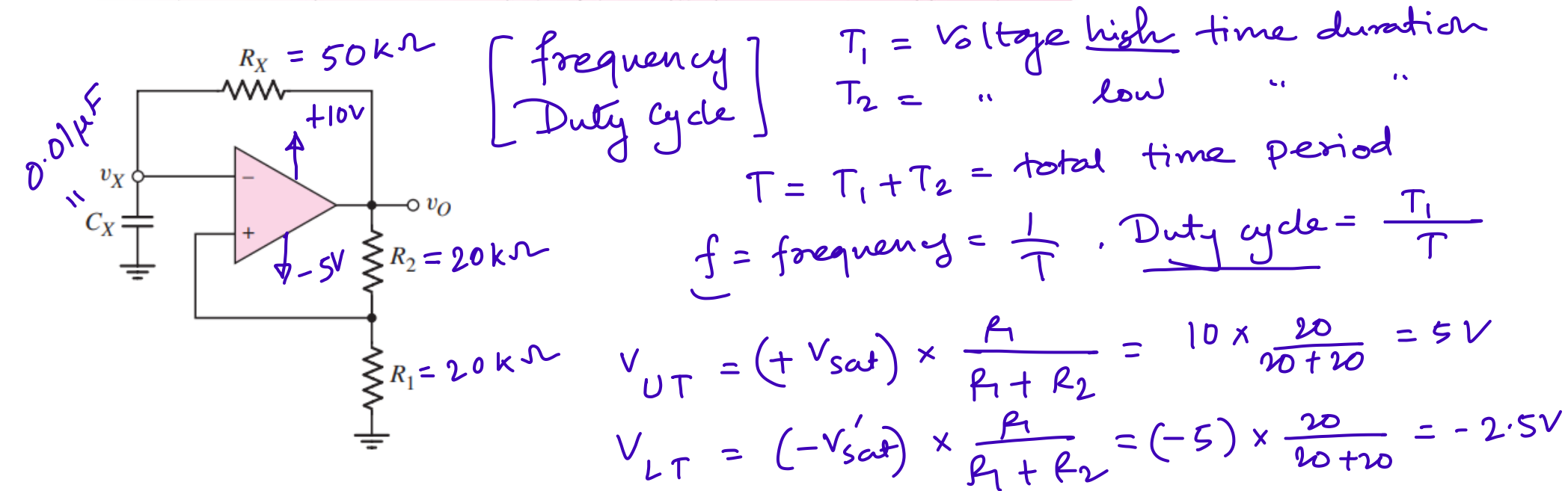EXERCISE PROBLEM

***Ex 15.8:** For the Schmitt trigger oscillator in Figure 15.35, the saturation output voltages are $+10\text{ V}$ and -5 V . $R_1 = R_2 = 20\text{ k}\Omega$, $R_X = 50\text{ k}\Omega$, and $C_X = 0.01\text{ }\mu\text{F}$. Determine the frequency of oscillation and the duty cycle. Sketch



Square Wave Generator

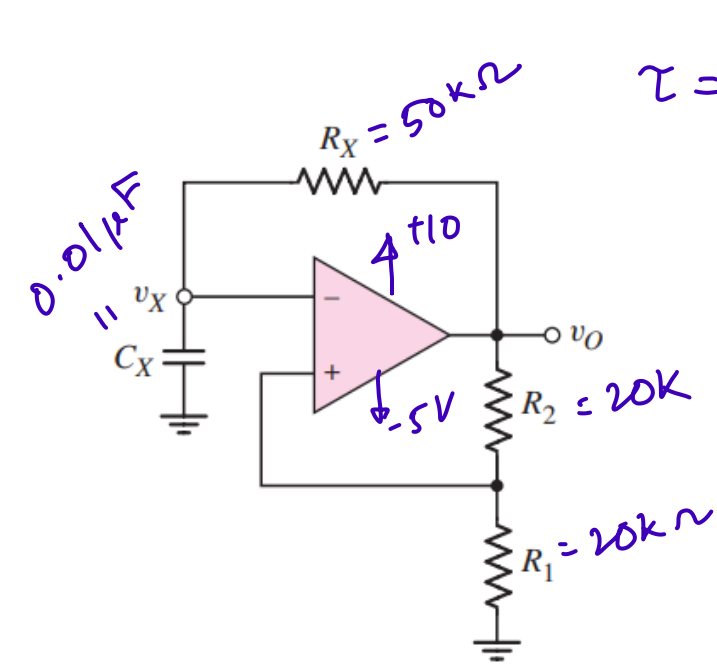

$$\tau = R_X C_X = 50 \times 10^3 \Omega \times 0.01 \times 10^{-6} \text{F} = 0.5 \text{ms}$$

$$T_1 = \tau \ln \left(\frac{+V_{\text{sat}} - V_{LT}}{V_{\text{sat}} - V_{UT}} \right) = 0.5 \text{ms} \ln \left[\frac{10 - (-2.5)}{10 - 5} \right] = 0.5 \text{ms} \ln(2.5)$$


$$T_2 = \tau \ln \left(\frac{-V_{\text{sat}} - V_{UT}}{-V_{\text{sat}} - V_{LT}} \right) = 0.5 \text{ms} \ln \left[\frac{-5 - 5}{-5 - (-2.5)} \right] = 0.5 \text{ms} \ln(4)$$

$$T = T_1 + T_2 = 0.5 \ln(2.5 \times 4) = 0.5 \ln(10)$$

$$f = \frac{1}{0.5 \ln(10)} = 0.868 \text{ kHz} = 868 \text{ Hz}$$

$$\text{Duty Cycle} = \frac{T_1}{T} = \frac{\ln(2.5)}{\ln(10)} \approx 39.1\%$$

Triangular Wave Generator

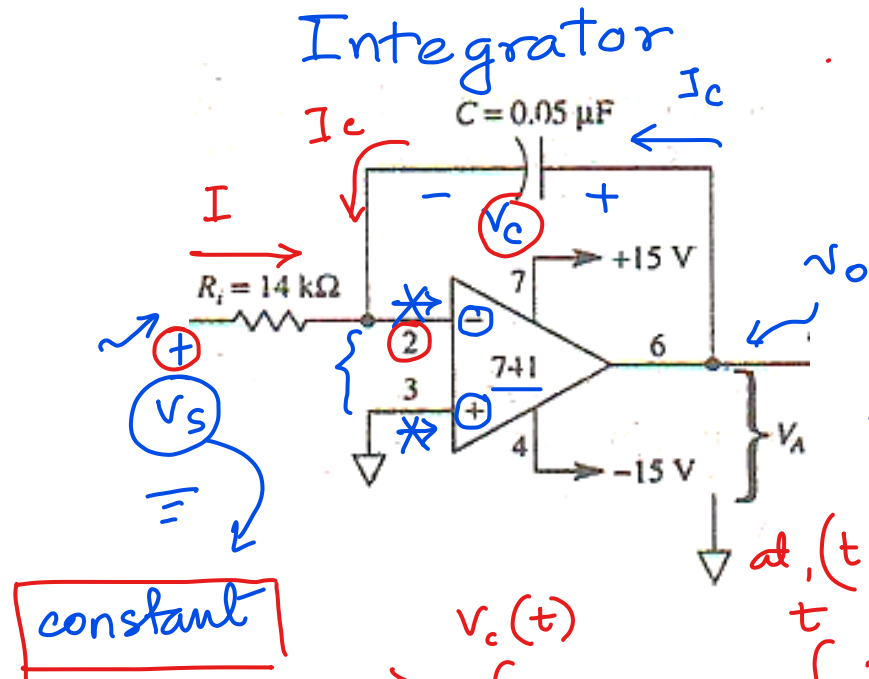

$$v^- = 0V$$

$$I = \frac{V_s}{R_i}, \quad I + I_c = 0$$

$$I_c = C \frac{dV_c}{dt} = -\frac{V_s}{R_i}$$

$$\Rightarrow \int dV_c = - \int \frac{V_s}{R_i C} dt$$



$$at, (t = t_1), V_c = V_{initial}, \quad V_c(t) = ? \quad \text{where } t > t_1$$

$$\Rightarrow \int_{V_{initial}}^{V_c(t)} dV_c = - \int_{t_1}^t \frac{V_s}{R_i C} dt \Rightarrow V_c(t) - V_{initial} = - \frac{V_s}{R_i C} (t - t_1)$$

$$\Rightarrow V_c(t) = V_{initial} - \frac{V_s}{R_i C} (t - t_1)$$

Triangular Wave Generator

Steady state condition

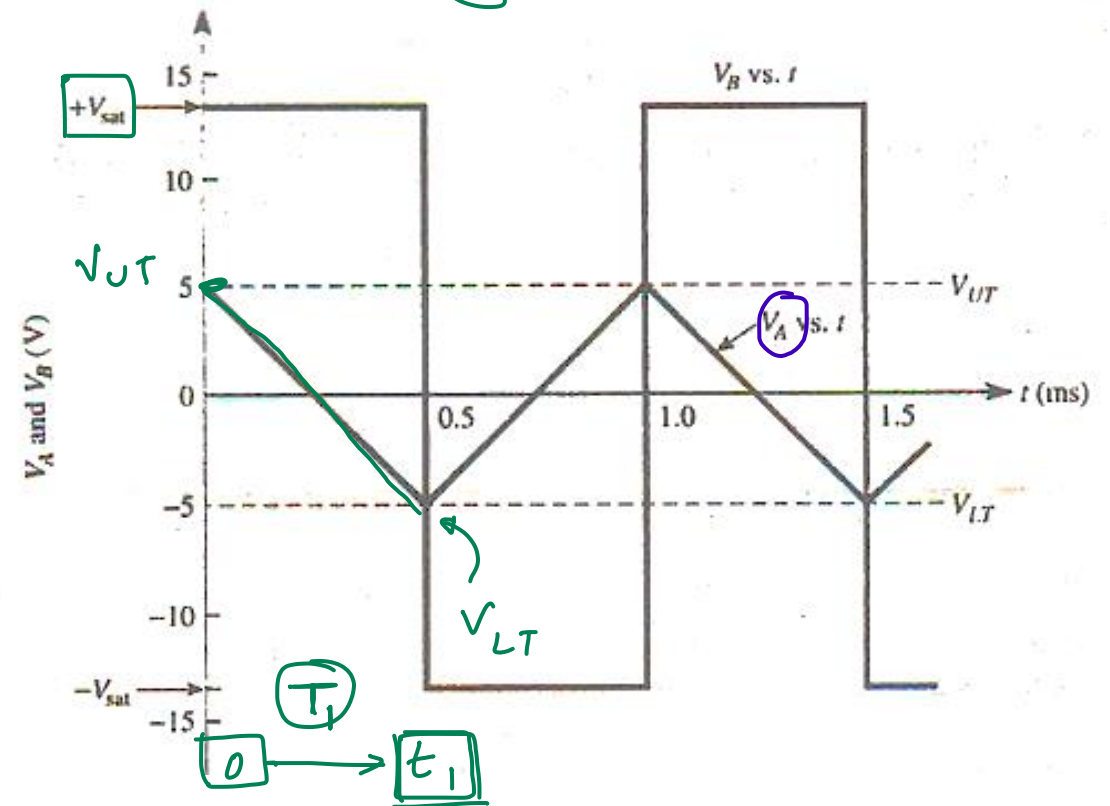
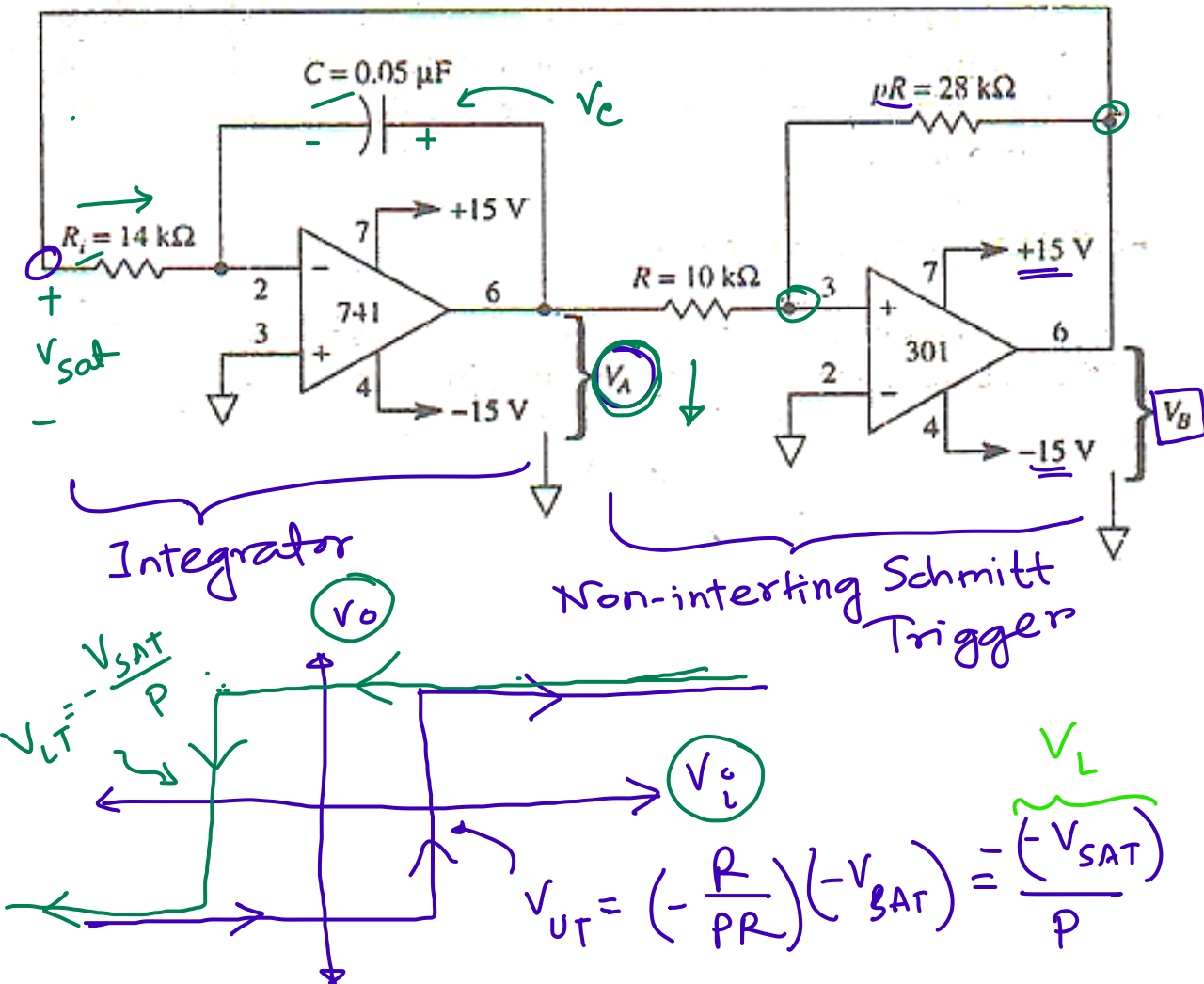


$$V_c(t) = V_{initial} - \frac{V_s}{R_i C} (t - t_{initial})$$

$$\Rightarrow V_{LT} = V_{UT} - \frac{V_{SAT}}{R_i C} (T_1) \Rightarrow T_1 = R_i C \left(\frac{V_{UT} - V_{LT}}{V_{SAT}} \right)$$

higher saturation voltage

Triangular Wave Generator

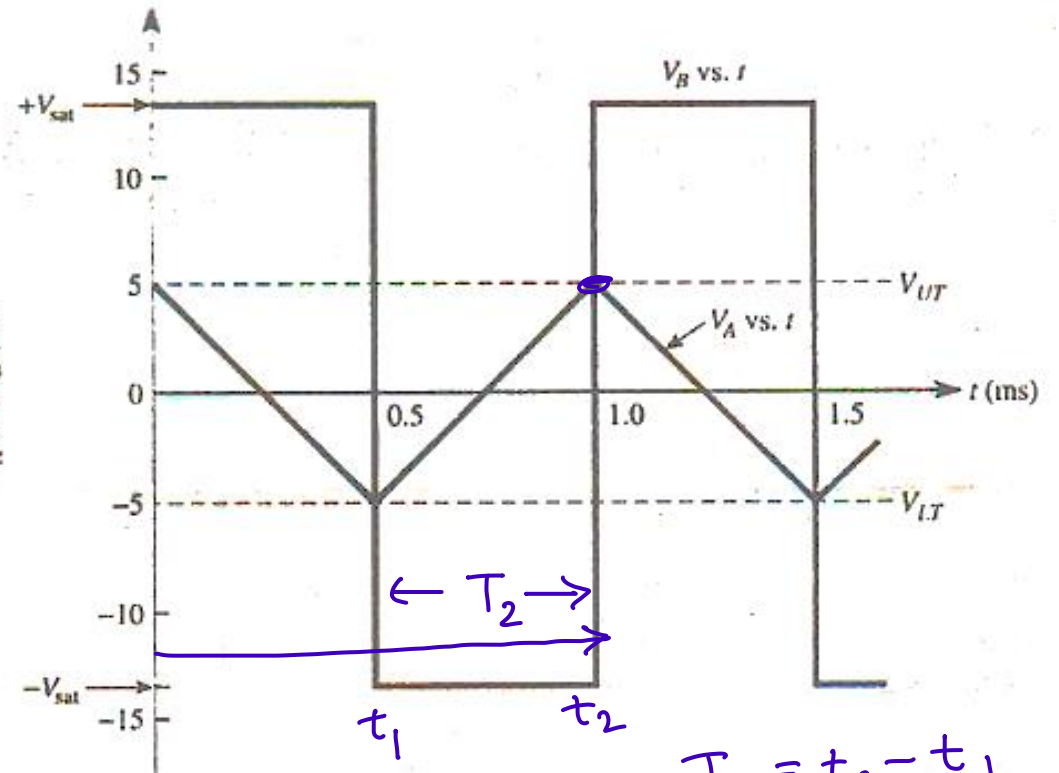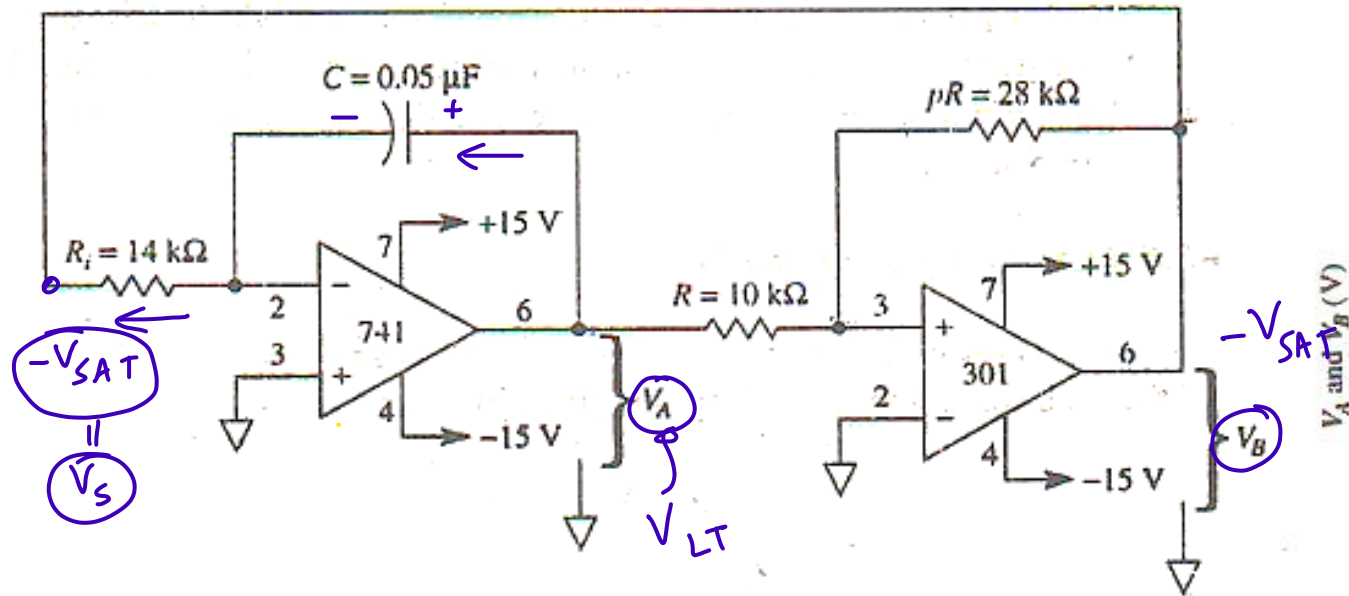

$$V_c(t) = V_{\text{initial}} - \frac{V_s}{R_i C} (t - t_{\text{initial}})$$

$$\Rightarrow \underbrace{V_c(t_2)}_{V_{UT}} = V_{LT} - \underbrace{\left(\frac{-V_{sat}}{R_i C} \right)}_{T_2} (t_2 - t_1) \Rightarrow$$

$$T_2 = \frac{(V_{LT} - V_{UT})}{(-V_{sat})} R_i C$$

lower saturation voltage

Triangular Wave Generator

Total Time period, $T = T_1 + T_2$

$$= \left(\frac{V_{UT} - V_{LT}}{+V_{SAT}} + \frac{V_{LT} - V_{UT}}{-V_{SAT}} \right) \times R_i C$$


frequency, $f = \frac{1}{T}$, $\pm V_{SAT} = 15$, $P = \frac{PR}{R} = \frac{28}{10} = 2.8$

$$\left[V_{UT} = -\frac{(-V_{SAT})}{P} \right] = -\frac{(-15)}{2.8} = 5.357V, \quad V_{LT} = -5.357V$$


$$T = \left(\frac{4 \times 5.357}{15} \right) \times 0.05 \mu \times 14K = 1ms. \quad \boxed{f = 1kHz}$$

$$f = \frac{P}{4R_i C}$$

Unipolar Triangular Wave Generator

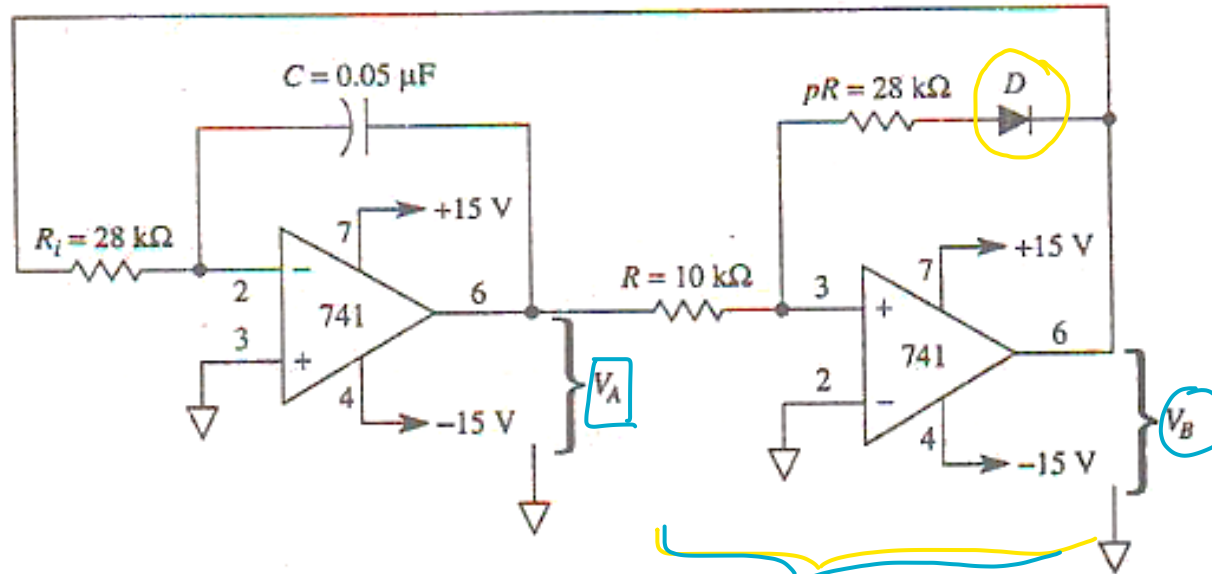


(a) Unipolar triangle-wave generator.

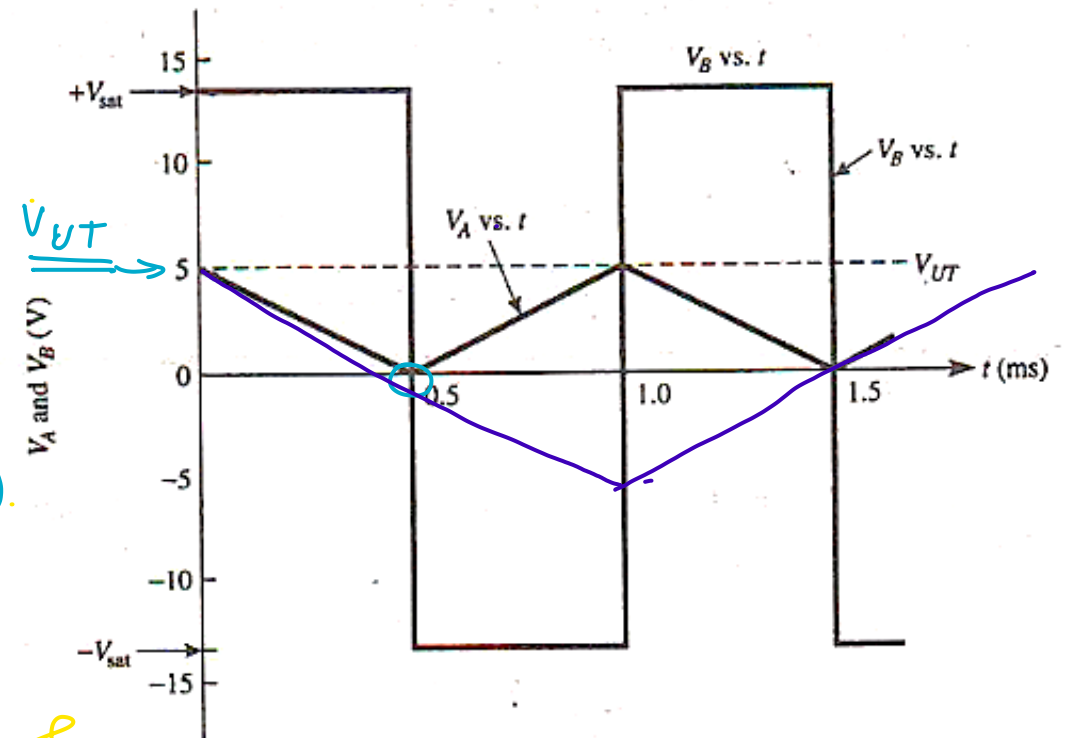

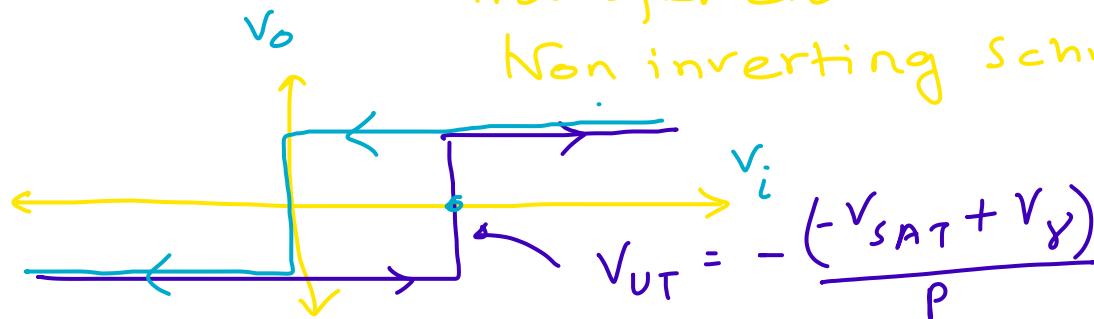(b) Waveshapes.

Transfer characteristics of
Non inverting Schmitt Trigger



Unipolar Triangular Wave Generator

Example 6-7 → Coughlin's

Find the approximate peak voltage and frequency for the unipolar triangle-wave generator in Fig.

Solution Calculate

$$p = \frac{pR}{R} = \frac{28 \text{ k}\Omega}{10 \text{ k}\Omega} = 2.8$$

Find the peak value of V_A from Eq.

$$V_{UT} = -\left(\frac{-V_{\text{sat}} + 0.6 \text{ V}}{p}\right) = -\left(\frac{-13.8 \text{ V} + 0.6 \text{ V}}{2.8}\right) \approx \underline{4.7 \text{ V}}$$

15 → 13.8 V
Conduction voltage of a diode

$$f = \frac{p}{2R_1 C} = \frac{2.8}{2(28 \text{ k}\Omega)(0.05 \text{ }\mu\text{F})} = 1000 \text{ Hz}$$

$2 \times \left(\frac{p}{4R_1 C}\right)$

Reference

- ✓ ☒ Chapter 6 of Operational Amplifiers and Linear Integrated Circuits by Coughlin & Driscoll
- ✓ ☒ Chapter 15 of Microelectronics Circuit Analysis by Donald Neamen