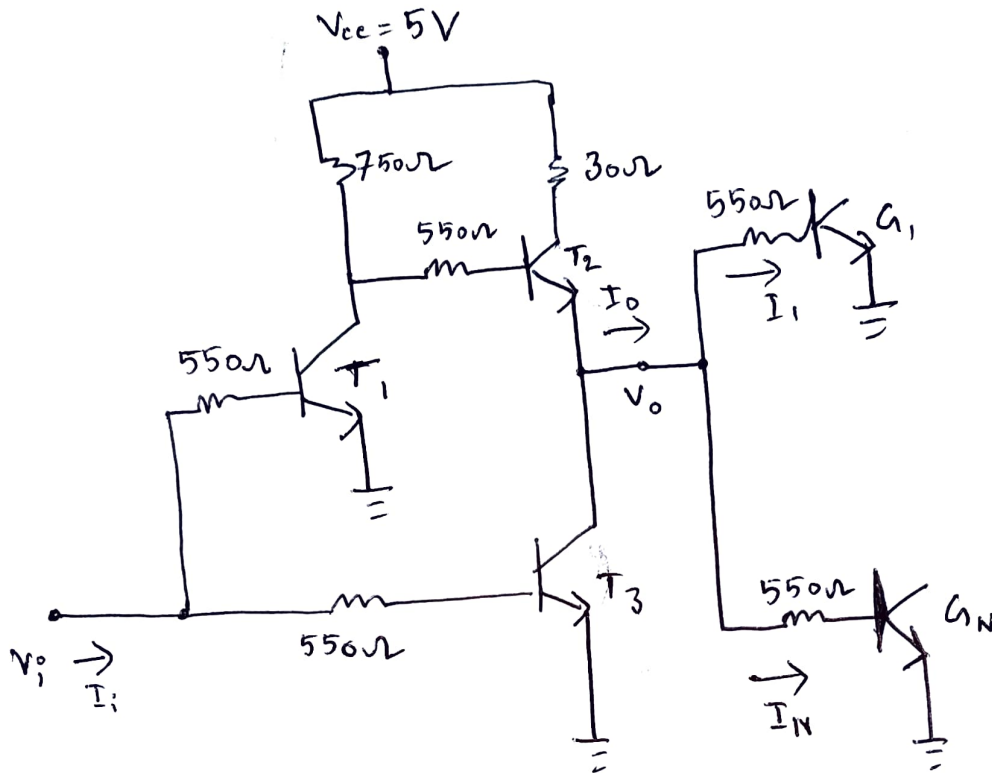


CSE350 (Quiz:1)

Name: Kazi Md. Al-Wakil

ID: 19301051

Section: 12



Here, ~~for~~

for case: 1,


$$V_i = 0V$$

So,  $T_1, T_3 \rightarrow$  Cut off

$T_2 \rightarrow$  Forward active

$T_2$  is in forward active because,

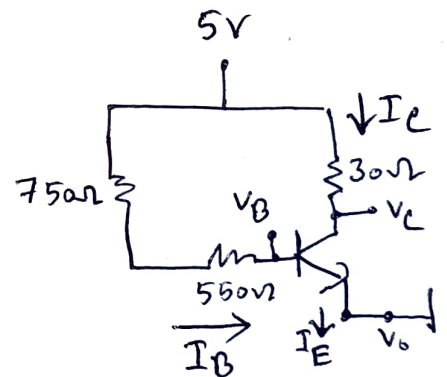We can see, The collector voltage of  $T_2$  is very small. So, the collector voltage is almost 5V. On the other hand,  $V_B$  is significantly lower than  $V_C$ .



So we can state that,

$$V_C > V_B$$

$$\Rightarrow V_B - V_C < 0$$

$$\Rightarrow V_{BC} < 0$$

And,

$$V_{BE} > 0.5$$

So,  $T_2$  transistor is in forward active mode.

So, we know,

$$I_C = \beta_F I_B$$

$$= 30 I_B$$

$$I_C = \alpha I_E$$

$$= \frac{\beta}{1+\beta} I_E$$

$$= \frac{30}{1+30} I_E$$

$$= \frac{30}{31} I_E$$


KCL,

$$I_E = I_B + I_C$$

$$= I_B + 30 I_B$$

$$= I_B (30+1)$$

$$= 31 I_B$$

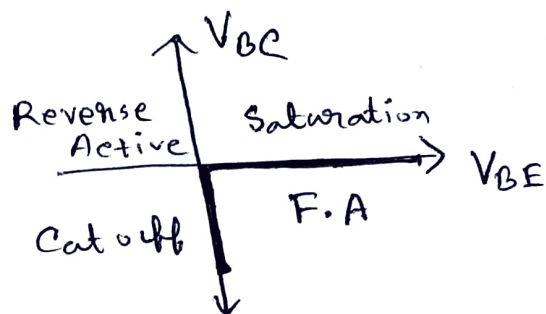

We also know,

$$V_{BE} = 0.7$$

$$\Rightarrow V_B - V_E = 0.7$$

$$\Rightarrow V_B = V_0 + 0.7 \quad [V_E = V_0]$$

~~70~~

Now,

$$I_B = \frac{5 - V_0 - 0.7}{1.3 \times 10^3}$$

$$= \frac{4.3 - V_0}{1.3 \times 10^3}$$

Now,

The output of driver circuit is low,

$$\text{So, } V_o = 3.3 = V_{OH}$$

$$\text{So, Max current supply} = 31 \times \frac{4.3 - \cancel{3.3}}{1.3} = 23.85$$

Individual demand load current,

$$I_1 = \frac{3.3 - 0.8}{0.55} = 4.545$$

$$\therefore \text{Maximum fanout} = \frac{23.85}{4.545} = 5.25$$

Case: 2

$$V_i = 5V$$

So,  $T_1, T_3 \rightarrow \text{Saturation}$

$$V_o = 0.2V$$

$$V_B(T_2) \approx 0.2V$$

$$V_E(T_2) \approx 0.2V$$

$$V_{BE}(T_2) = 0V < 0.5V$$

$T_2 \rightarrow \text{cut off}$

So,  $G_1, G_2, \dots, G_N$  in cutoff

demand current = 0

$$\text{Maximum fanout} = \frac{0}{0} = \infty$$

Any number of fanout is valid.

$$\text{Maximum fanout} = \cancel{21} 5$$

(b)

If the input is 0.2V and 2 load circuits connected to the driver, the total power dissipation will be in the driver:

If input is 0.2V.

then  $T_1, T_3$  will be in cutoff  
 $T_2$  " " " forward active

So, the,  $V_o = V_{OH} = 3.3$

$$\text{So, } I_B = \frac{4.3 - 3.3}{1.3} = 0.769 \text{ mA}$$

$$I_C = \beta_0 I_B = 23.077 \text{ mA}$$

$$I_E = 31 I_B = 23.839 \text{ mA}$$

So, power dissipation :  $\Delta V I_E$

$$= (0.2 - 0) 23.839 \text{ mA}$$

$$= 4.77 \text{ mW.}$$

(Am)