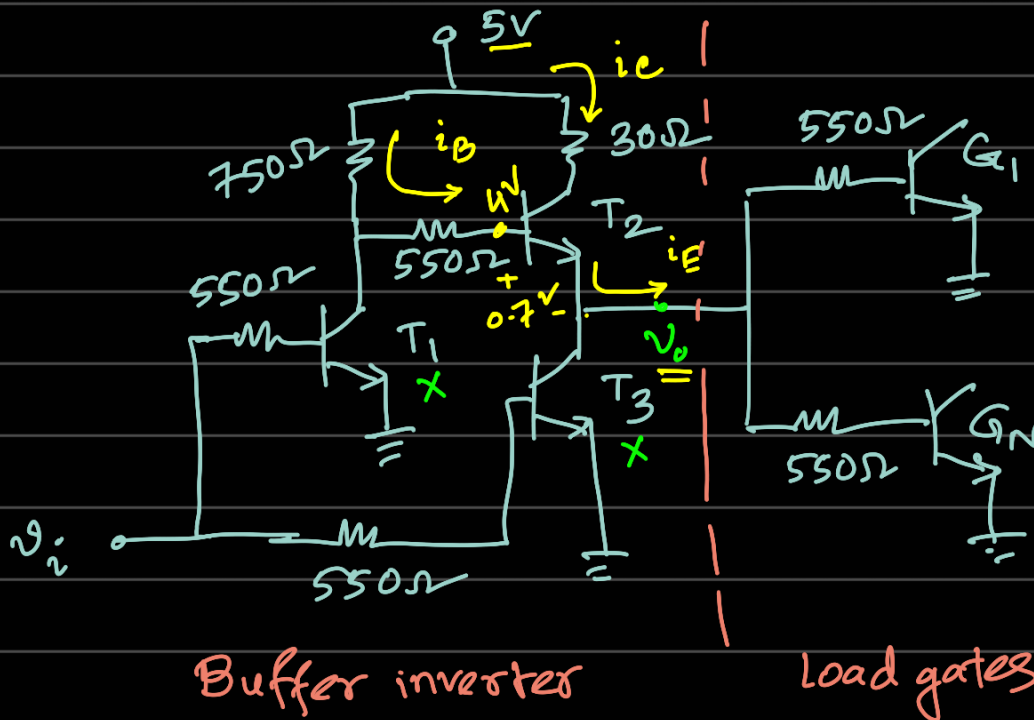


Quiz 1 Solution:



$$V_{OH} = 3.3V$$

$$V_{OL} = 0.2V$$

$$V_{BE(sat)} = 0.8V$$

$$V_{CE(sat)} = 0.2V$$

$$V_f = 0.5V$$


$$\beta_F = 30$$

@ Maximum fanout calculation:

Case 1: $v_i = 5V$. $T_3 \rightarrow$ saturation. $v_o \rightarrow 0.2V$. $G_1 \dots G_N \rightarrow$ cutoff mode. Demand current = 0. supply current = 0. fanout = ∞ .

Case 2: $v_i = 0.2V$. $T_1, T_3 \rightarrow$ cutoff. $T_2 \rightarrow$ forward active.

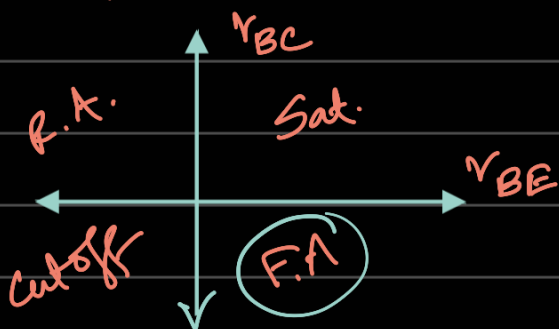Because collector terminal is connected to 5V with very small resistance compared to the base terminal of T_2 transistor. Thus $V_B < V_C \Rightarrow V_{BC} < 0$.




Allowed value of $v_o = V_{OH} = 3.3V$

$$i_B = \frac{5 - 4}{750 + 550} = \frac{1}{1.3} = 0.7923 \text{ mA}$$

$$i_C = \beta_F i_B = 0.7923 \times 30 = 23.077 \text{ mA}$$

$$i_E = i_C + i_B = 23.846 \text{ mA}$$

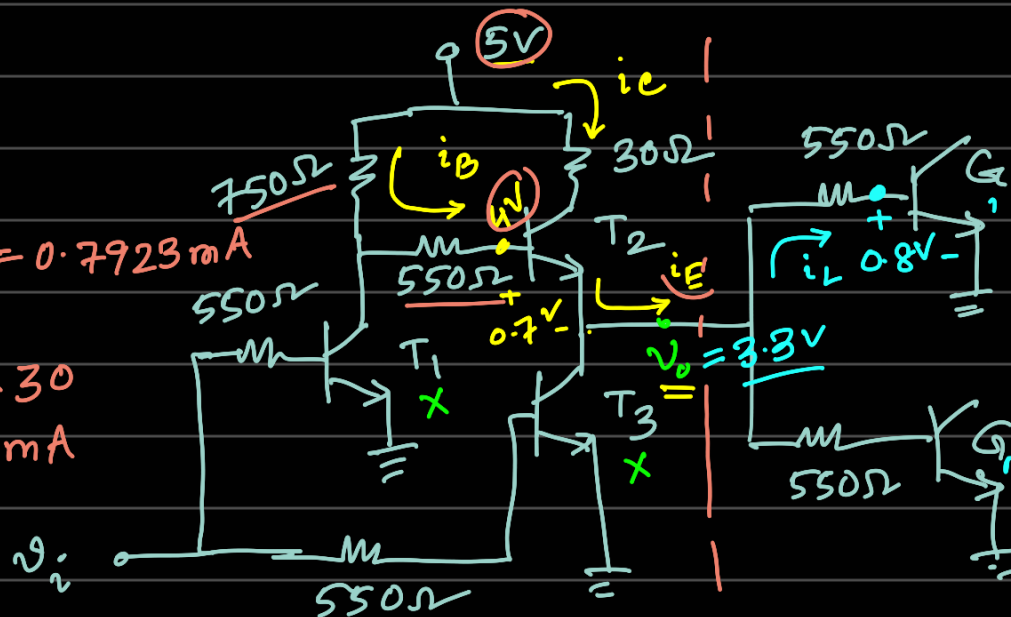

G_1, G_2, \dots, G_N are in saturation mode.

$$\text{individual demand current} = \frac{3.3 - 0.8}{0.55} = 4.5454 \text{ mA}$$


$$\text{Max. fanout} = \left\lfloor \frac{\text{supply current}}{\text{demand current}} \right\rfloor = \left\lfloor \frac{23.846}{4.5454} \right\rfloor = 5$$

(b) $i_B = \frac{(5 - (V_{BE} + 0.7))}{1.3}$, $[i_E = (\beta + 1)i_B] \rightarrow \text{supply}$

$$\left[i_L = \frac{v_o - 0.8}{0.55} \right] \rightarrow \text{individual demand.}$$

$$(30+1) \frac{(5 - (V_o + 0.7))}{1.3} = 2 \times \left(\frac{V_o - 0.8}{0.55} \right) \quad \uparrow \quad \underline{5V}$$

$$\Rightarrow v_o = 3.8368 \text{ V}$$

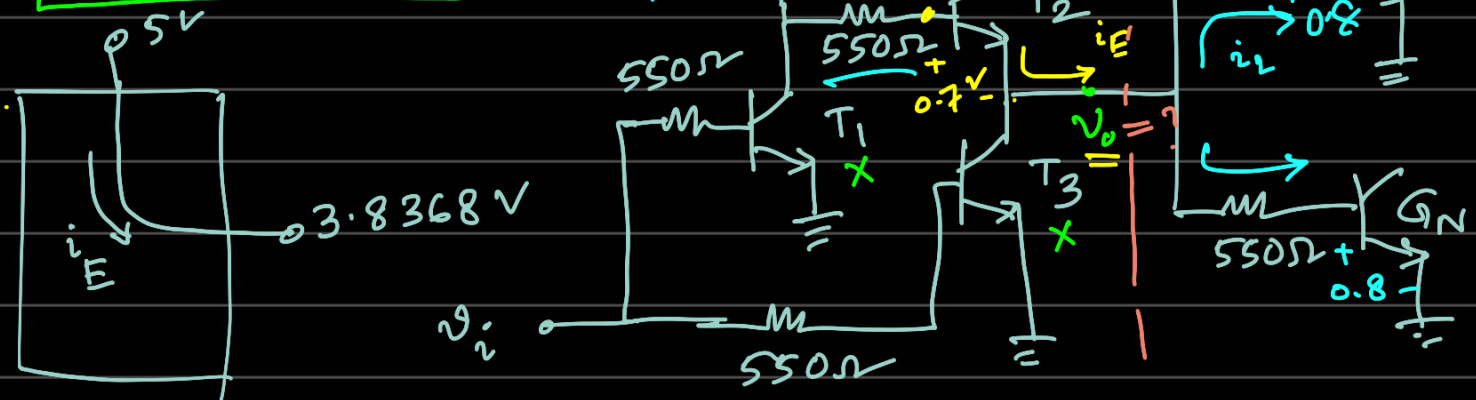

$$I_E = 31 \times \left(\frac{5 - 3.8368 - 0.7}{1.3} \right) = 1.1043 \text{ mA}$$

$$\text{Power dissipation} = (5 - 3.8368) \times 1.1043$$
$$= 12.84 \text{ mW}$$

Quiz 2 solution:

@ Noise margin low calculation

Normal operation:


$$V_1 = 0.1V, V_2 = 18V$$

$P_1 \rightarrow ON, D_2 \rightarrow OFF.$

$Q_1, D_3, Q_0 \rightarrow OFF.$

Malfunction will occur if Q_1, D_3, Q_0 turns on.

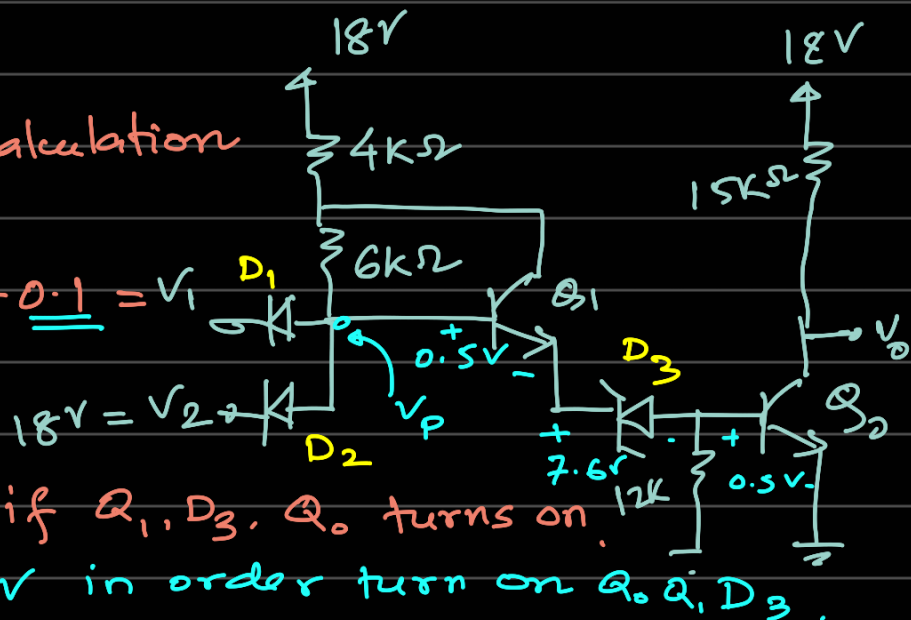
$$V_p = 0.5 + 7.6 + 0.5 = 8.6V \text{ in order turn on } Q_0, Q_1, D_3$$



However, without noise v_p has voltage. $0.1 + 0.7 = 0.8V$

$$0.8 + V_N = 8.6V \Rightarrow V_N = 8.6 - 0.8 = \boxed{7.8V}$$

(b)

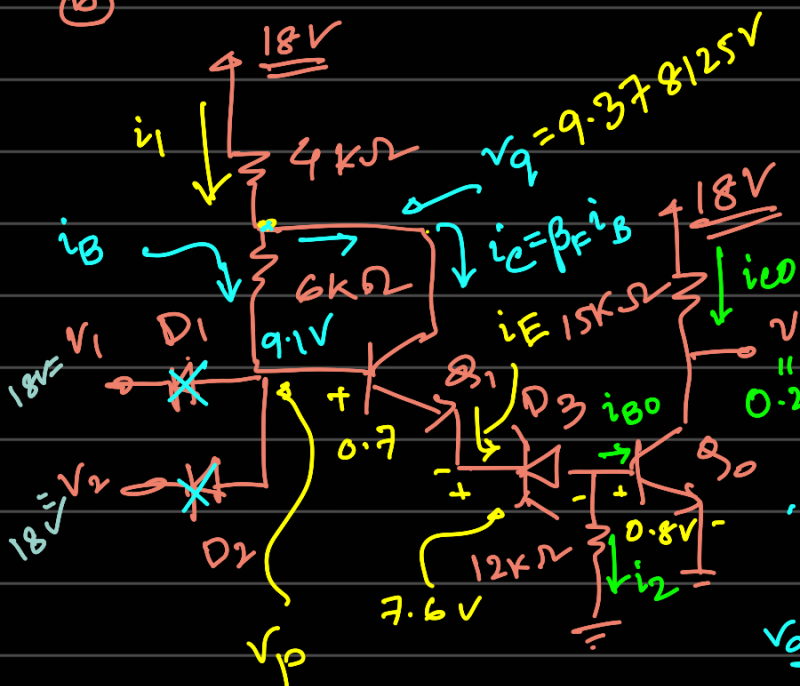

$$V_1 = V_2 = 18V.$$

$D_1, D_2 \rightarrow \text{OFF}.$

Q_1, D_3 and Q_4 are ON.

For Q_1 , $V_E > V_B \Rightarrow V_{BC} < 0$

$\therefore Q_1$ is in forward active mode.

Q_4 is in saturation mode.

$$\therefore V_p = 0.8 + 0.7 + 7.6V = 9.1V$$

$$\frac{V_q - 18}{4} + \frac{V_q - 9.1}{4} + 30 \times \frac{V_q - 9.1}{4} = 0$$


$$\Rightarrow V_q = 9.378125V$$

$$i_1 = i_C + i_B = i_E$$

$$= \left(\frac{18 - 9.378125}{4k} \right) = 1.437 \text{ mA}, \quad i_2 = \frac{0.8 - 0}{12k} = 0.0333 \text{ mA}$$

$$\therefore i_{B0} = i_1 - i_2 = 1.4036 \text{ mA}, \quad i_{C0} = \frac{18 - 0.2}{15k} = 1.18667 \text{ mA}.$$

(i) Power dissipation calculation:

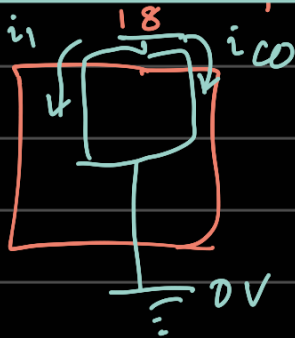

$$P = (18 - 0) \times (i_1 + i_{C0})$$

$$= 18 \times (1.437 + 1.18667)$$

$$\boxed{P = 47.226 \text{ mW}}$$

(ii) minimum value of β . $\beta_{\min} = \beta_{\text{forced}}$

$$\boxed{\beta_{\min} = \frac{i_{C0}}{i_{B0}} = 0.84544}$$