

CSE 350

LAB: 5

Name: Kazi Md. Al-Wakil

ID: 19301051

Section: 12

Here,

$$\text{Frequency (theoretical)}: \frac{1}{4 * R_1 * C} \times \frac{R_2}{R_3}$$

Given that,

$$R_1 = 10 \text{ k}\Omega$$

$$R_2 = 10 \text{ k}\Omega$$

$$R_3 = 4 \text{ k}\Omega$$

$$C = 0.4 \mu\text{F}$$

$$= \frac{1 \times 10 \times 10^3}{4 \times 10 \times 10^3 \times 0.4 \times 10^{-6} \times 4 \times 10^3}$$
$$= 156.25 \text{ Hz}$$

Now, From photo's:

Frequency (practical):

$$\text{Experimental time period, } t = (150 - 143.3) \times 10^{-3}$$
$$= 6.7 \text{ ms}$$

$$\text{Now, frequency, } f = \frac{1}{t} = \frac{1}{6.7 \times 10^{-3}} = 149.254 \text{ Hz}$$

Data table:

Theoretical frequency	Experimental time period, T (ms)	Experimental frequency F (Hz)
156.25	6.7	149.254

Report:

① Output wave shape at point A:

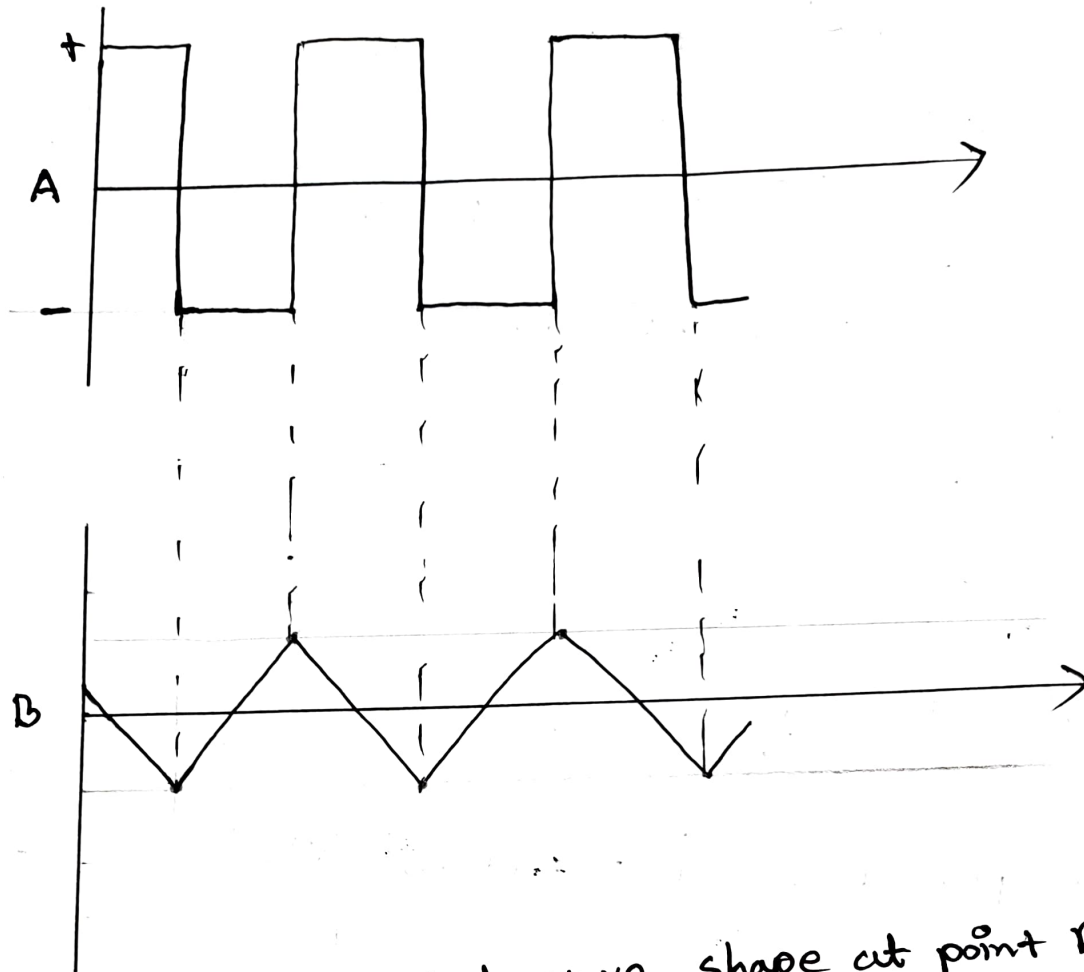


Fig: Output wave shape at point B

Date:/...../.....

② There are two sections of the triangular wave oscillator.
They are:

① Schmitt

② Op-amp integrator.

Schmitt produces a square shaped wave at point A. Also, Op-amp integrator produces a triangular wave at point B. Depending on the capacitor there is also a capacitor as output.

Now, schmitt trigger circuit has two thresholds.

① Upper

② lower


When current flows through the lower part, it creates high square shape as output and when current flows through the ~~lower part~~ higher part, it creates a full square shape.

In op-amp integrator, when we get lower signal from output A, it goes to the upper signal at B. Similarly when it gets higher signal from output A, it goes to the lower signal at B. These up and downs creates the triangular shape.

- ③ Yes, the integrator circuit can be implemented by with an inductor.

~~Inductor~~:

Here,

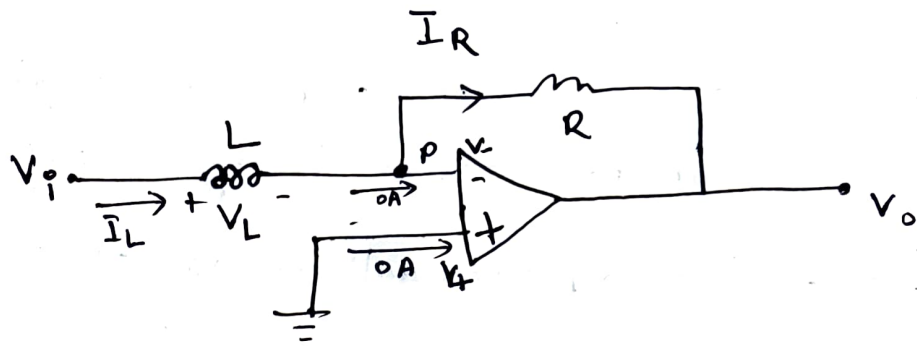

$$I_p = \frac{0 - V_o}{R}$$

$$= \frac{-V_o}{R} ; \left. \begin{matrix} V^- = 0 \\ V^+ = 0 \end{matrix} \right\} \text{Virtual ground concept}$$

KCL,

$$I_L = 0 + I_R = I_R$$

$$V_L = V_i - 0 = V_i$$

$$\Rightarrow V_L = L \frac{dI_L}{dt}$$

$$= L \frac{dI_R}{dt}$$

$$\therefore V_i = V_L = - \frac{L}{R} \times \frac{dV_o}{dt}$$

$$\Rightarrow \frac{-R}{L} V_i = \frac{dV_o}{dt}$$


$$\Rightarrow \int \frac{dV_o}{dt} \times dt = - \int \frac{R}{L} V_i dt$$

$$\Rightarrow V_o = - \int \frac{R}{L} V_i dt. \quad (\text{Ans})$$


R = Negative feedback Resistance
 V_i = Input voltage
 V_o = Output "
 L = inductance.




Schematic Capture X

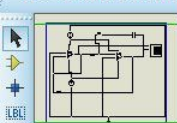

P L DEVICES

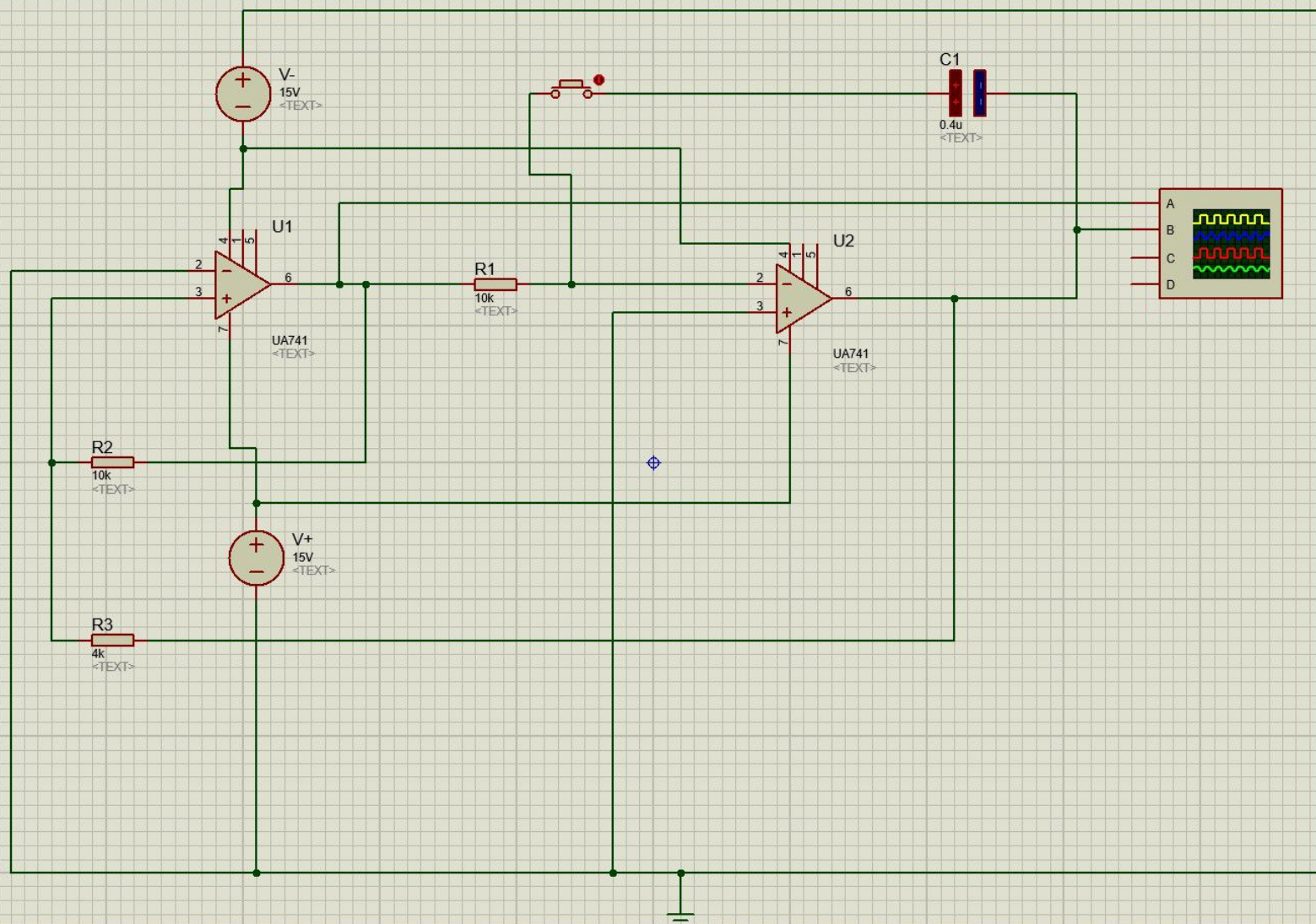BUTTON
CAPACITOR
RES
UA741
VSOURCE

Digital Oscilloscope

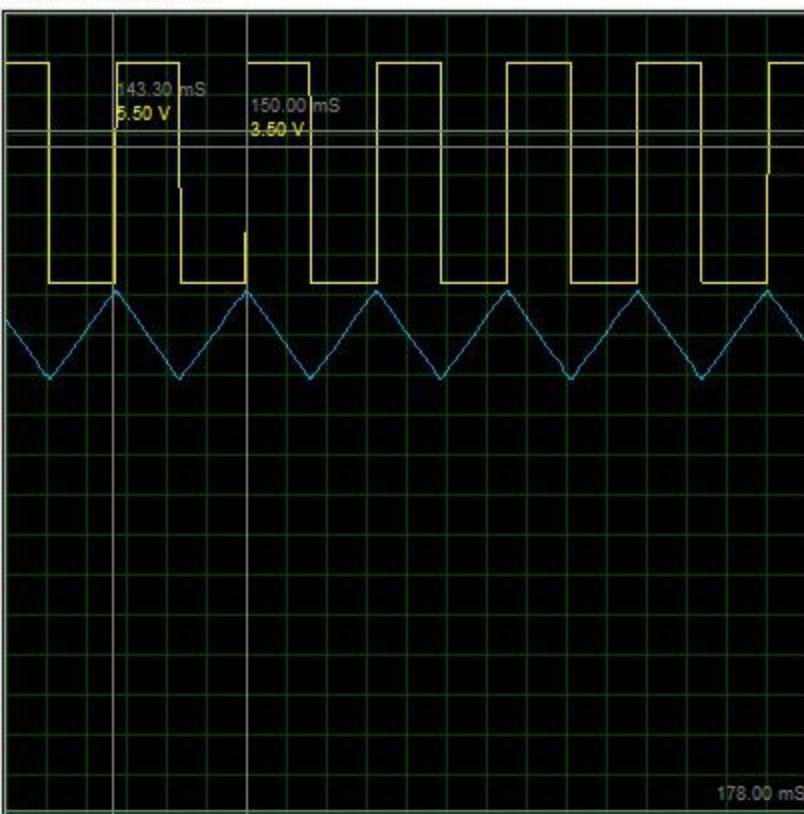

Trigger

Level: -10, 0, 10

AC DC

Auto One-Shot Cursors

Source: A B C D

Channel A

Position: 110, 120, 130

AC DC GND OFF

Invert A+B

5 V 5 mV

Channel C

Position: -210, -200, -190

AC DC GND OFF

Invert C+D

5 V 5 mV

Horizontal

Source: A B C D

Position: > -1380 >

200 ms 2m 0.5 μs

Channel B

Position: 30, 40, 50

AC DC GND OFF

Invert

5 V 5 mV

Channel D

Position: -210, -200, -190

AC DC GND OFF

Invert

5 V 5 mV