

P L DEVICES

RES


SW-SPDT

UA741

VSOURCE




0°

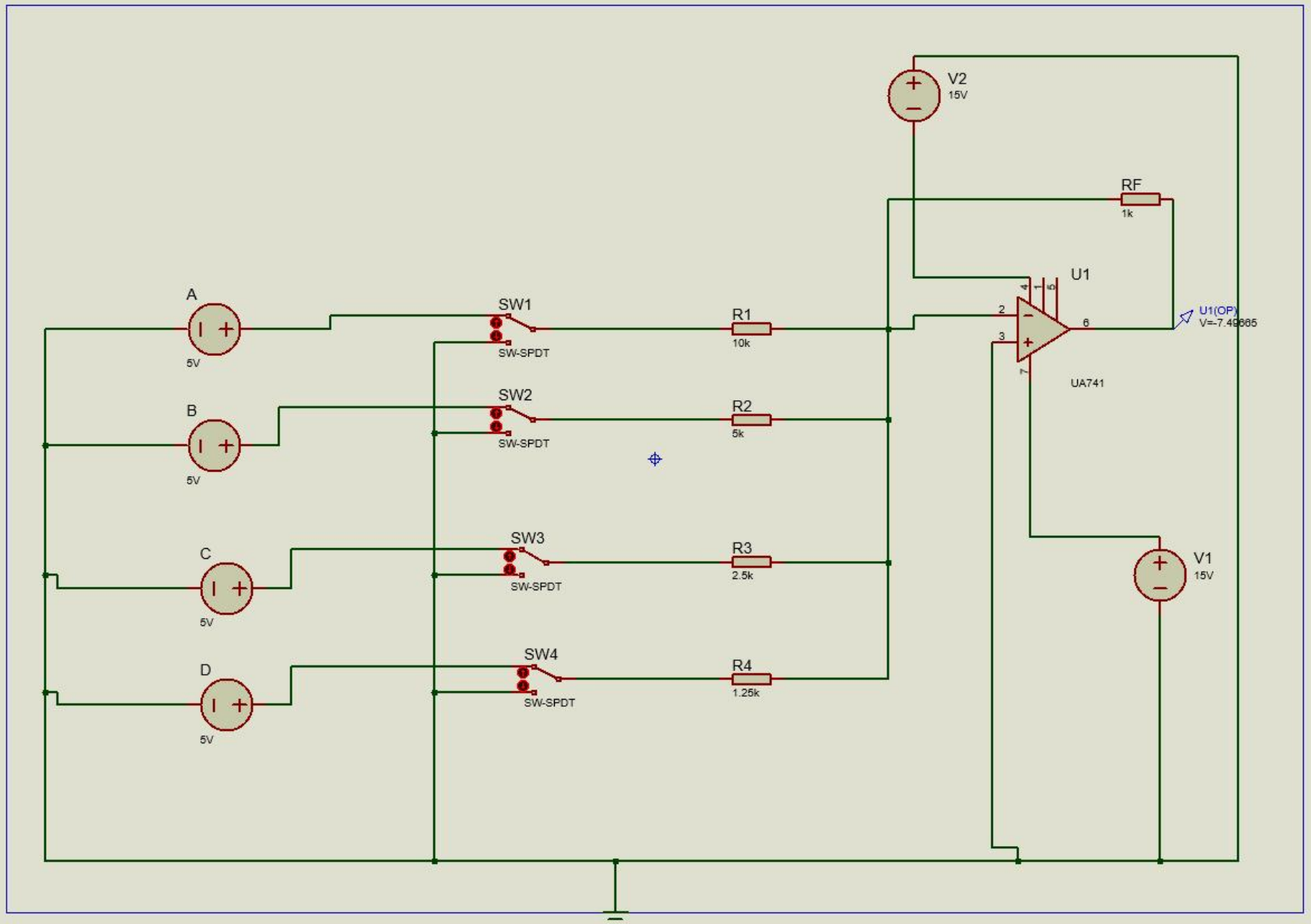



Schematic Capture X

 


P L DEVICES

RES

SW-SPDT

UA741

VSOURCE

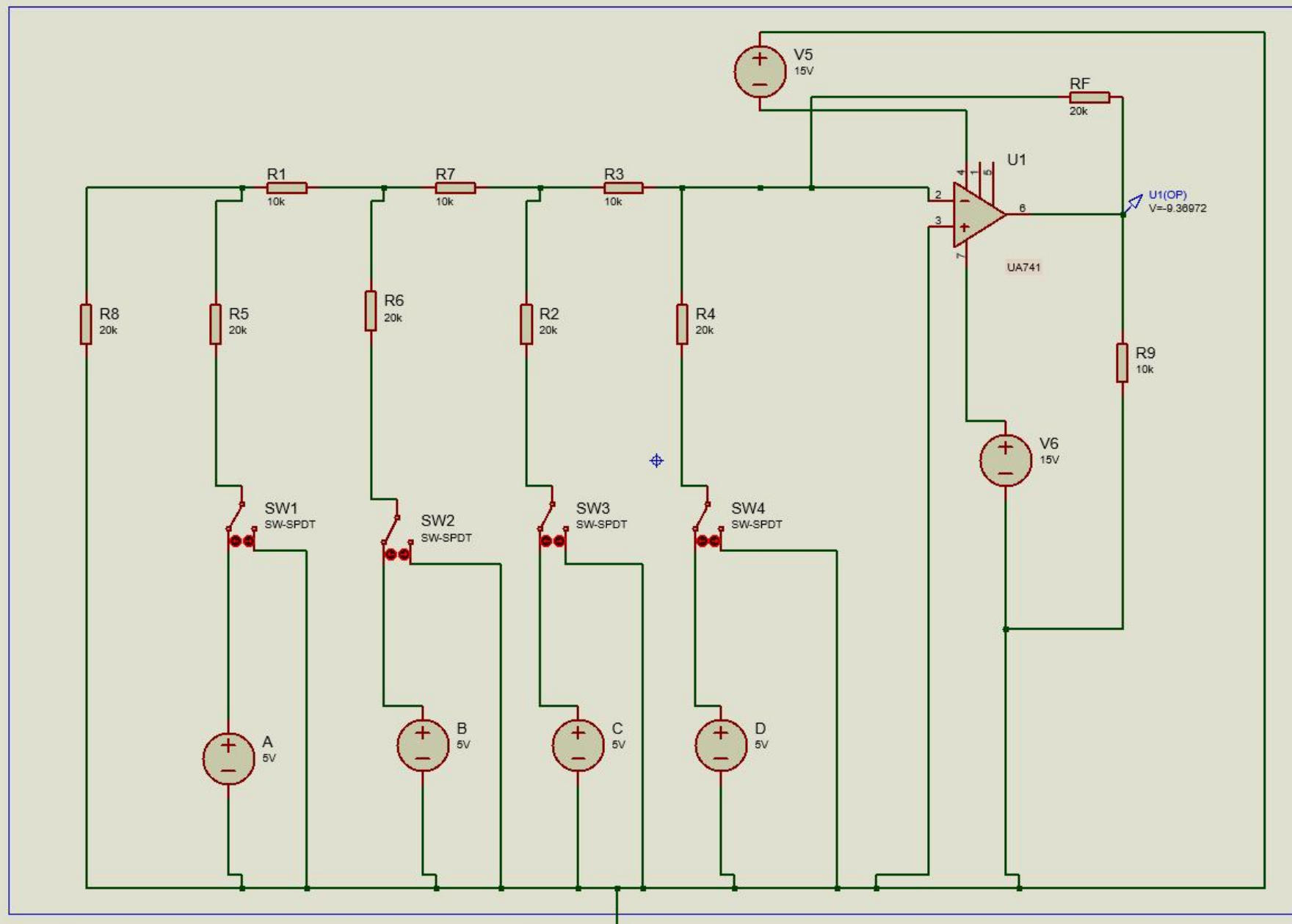

kh. Fardin Zubair Nafis

19301007 { Sec: 009 } Lab: 04

CSE-330.

Circuit 01

| Input Configuration | A | B | C | D | Output (Vo) |
|---------------------|---|---|---|---|------------------|
| | 0 | 0 | 0 | 0 | ≈ 0.0027 |
| 1 | 0 | 0 | 0 | 5 | ≈ 0.497 |
| 2 | 0 | 0 | 5 | 0 | ≈ 0.997 |
| 3 | 0 | 0 | 5 | 5 | ≈ 1.497 |
| 4 | 0 | 5 | 0 | 0 | ≈ 1.997 |
| 5 | 0 | 5 | 0 | 5 | ≈ 2.497 |
| 6 | 0 | 5 | 5 | 0 | ≈ 2.997 |
| 7 | 0 | 5 | 5 | 5 | ≈ 3.497 |
| 8 | 5 | 0 | 0 | 0 | ≈ 3.997 |
| 9 | 5 | 0 | 0 | 5 | ≈ 4.497 |
| 10 | 5 | 0 | 5 | 0 | ≈ 4.997 |
| 11 | 5 | 0 | 5 | 5 | ≈ 5.497 |
| 12 | 5 | 5 | 0 | 0 | ≈ 5.997 |
| 13 | 5 | 5 | 0 | 5 | ≈ 6.497 |
| 14 | 5 | 5 | 5 | 0 | ≈ 6.997 |
| 15 | 5 | 5 | 5 | 5 | ≈ 7.497 |

19301007

Circuit 02

| Input voltage combination | D | C | B | A | Output voltage (V) |
|---------------------------|---|---|---|---|--------------------|
| 1 | 0 | 0 | 0 | 0 | +0.0049 |
| 2 | 0 | 0 | 0 | 5 | -0.620 |
| 3 | 0 | 0 | 5 | 0 | -1.245 |
| 4 | 0 | 0 | 5 | 5 | -1.869 |
| 5 | 0 | 5 | 0 | 0 | -2.493 |
| 6 | 0 | 5 | 0 | 5 | -3.119 |
| 7 | 0 | 5 | 5 | 0 | -3.744 |
| 8 | 0 | 5 | 5 | 5 | -4.369 |
| 9 | 5 | 0 | 0 | 0 | -4.9948 |
| 10 | 5 | 0 | 0 | 5 | -5.619 |
| 11 | 5 | 0 | 5 | 0 | -6.244 |
| 12 | 5 | 0 | 5 | 5 | -6.869 |
| 13 | 5 | 5 | 0 | 0 | -7.494 |
| 14 | 5 | 5 | 0 | 5 | -8.1198 |
| 15 | 5 | 5 | 5 | 0 | -8.744 |
| 16 | 5 | 5 | 5 | 5 | -9.369 |

Report:

① In both circuit of D2A converter, we cannot get the higher output less than 15V and a higher than 15V. ~~Because~~ Because, in both circuit of D2A converter, -15V and +15V are bias voltage and so output will be between them.

② for both D2A converter
 \therefore input is 4 bits; \therefore full step output $= 2^4 - 1$
 $= 15$ steps.

Binary weighted resistor:






$$\left. \begin{array}{l} \text{Step size} = -0.497 \\ \text{full scale} = -7.497 \end{array} \right\} \therefore \text{resolution} = \frac{-0.497}{-7.497} = 0.0663 \text{ V}$$

R/2R D2A:



$$\left. \begin{array}{l} \text{step size} = -0.62 \\ \text{full scale} = -9.369 \end{array} \right\} \text{resolution} = \frac{-0.62}{-9.369} = 0.0661 \text{ V}$$

② if we choose, 0005 - 3 where A is 5V (high)
 B, C, D is (low) 0V.

    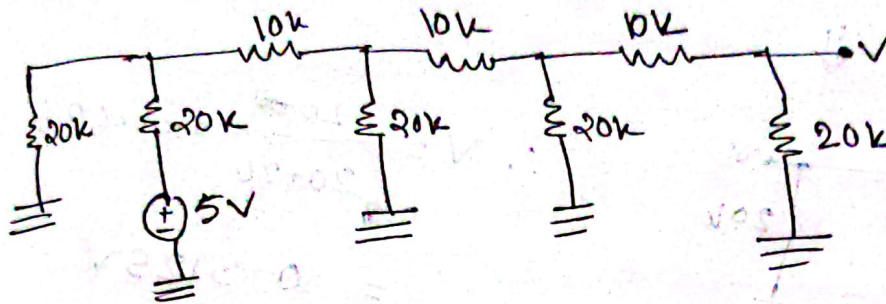Applying source transformation in this circuit




10/30/2017

  

$$\therefore V = \frac{20}{20+20} \times 0.625 = 0.3125V$$

Now,

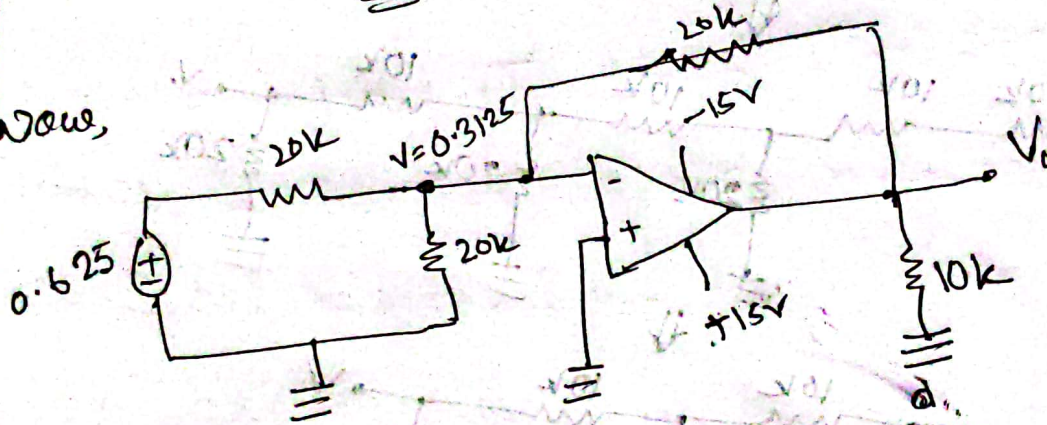

$$\therefore V_o = - \left\{ \left(\frac{20}{20} \times 0.625 \right) + \frac{20}{20} \times 0 \right\} \left[\text{Inv. adder Amp} \right]$$

$$= -0.625 \approx -0.62V$$

from, proteus, circuit 2, we got $-0.62V$ (for 0.005 OeB A)
and from calculation, we got -0.625 which is almost same.

for Circuit 01

19301007

④ Last 2 digit of ID = 07 = $0 + 7 = 7V = \text{high}$
Low = 0V.

| Input Configuration | D | C | B | A | Output v_o |
|---------------------|---|---|---|---|--------------|
| 1 | 0 | 0 | 0 | 0 | 0.007 |
| 2 | 0 | 0 | 0 | 1 | -0.697 |
| 3 | 0 | 0 | 1 | 0 | -1.397 |
| 4 | 0 | 0 | 1 | 1 | -2.097 |
| 5 | 0 | 1 | 0 | 0 | -2.797 |
| 6 | 0 | 1 | 0 | 1 | -3.497 |
| 7 | 0 | 1 | 1 | 0 | -4.197 |
| 8 | 0 | 1 | 1 | 1 | -4.897 |
| 9 | 1 | 0 | 0 | 0 | -5.596 |
| 10 | 1 | 0 | 0 | 1 | -6.297 |
| 11 | 1 | 0 | 1 | 0 | -6.997 |
| 12 | 1 | 0 | 1 | 1 | -7.697 |
| 13 | 1 | 1 | 0 | 0 | -8.397 |
| 14 | 1 | 1 | 0 | 1 | -9.097 |
| 15 | 1 | 1 | 1 | 0 | -9.796 |
| 16 | 1 | 1 | 1 | 1 | -10.496 |

10301007

⑤ when, $R_F = 1k\Omega$; Input for 0000 $\Rightarrow V_0 = 0.0027V$
 " " 0001 $\Rightarrow V_0 = -0.4097V$

$$\therefore \text{step size} = -0.4097 \approx 0.5V$$


when, $R_F = 3k\Omega$, input for 0000 $\Rightarrow V_0 = 0.006V$
 input " 0001 $\Rightarrow V_1 = -1.49V$

$$\therefore \text{step size} = -1.49 \approx 1.5V$$

So, if we increase R_F 3 times, step size also increase 3 times. So, if R_F increases, then step size also increases.

10301007

 Input-output graph for Binary weighted Resistor D2A



19301007.

