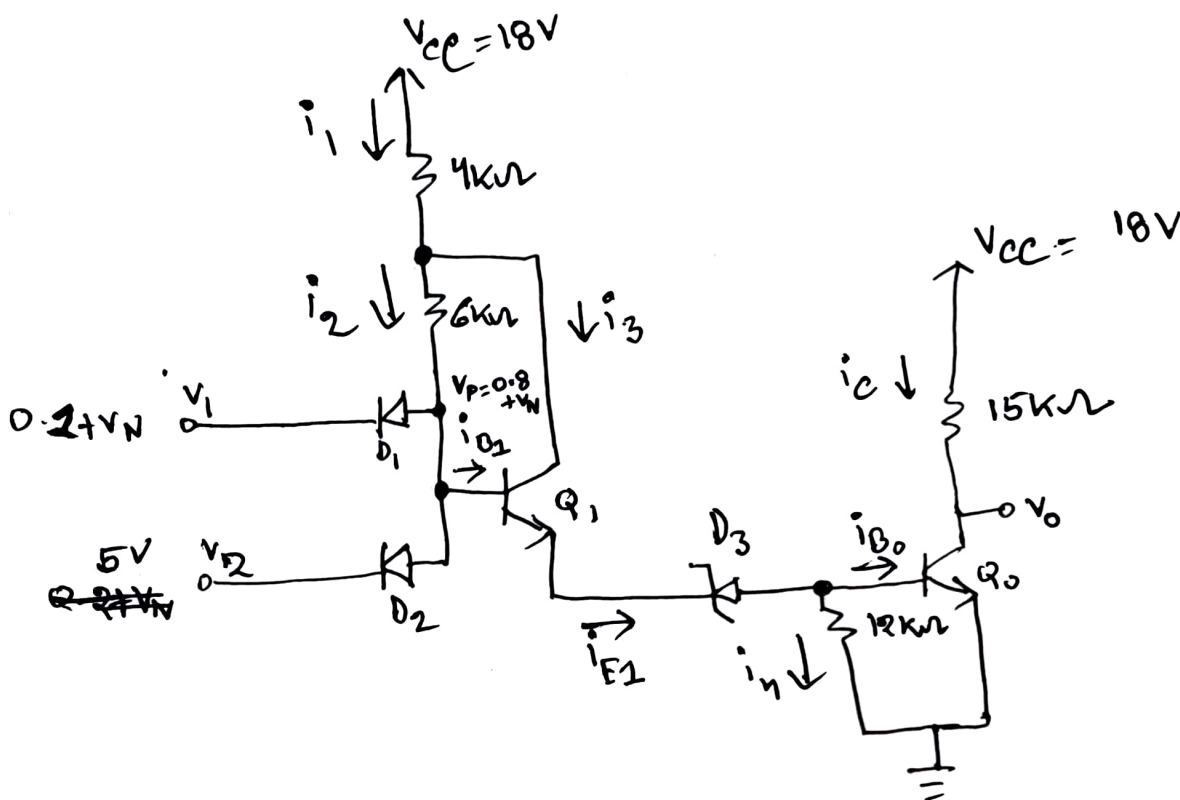


Name: Kazi Md. Al-Wakil

ID: 19301051

Sec: 12



Given that,

$$V_D (\text{diode}) = 0.6V$$

$$V_D (\text{transistor}) = 0.5V$$

$$V_D (\text{conducting voltage}) = 0.7V$$

$$V_{Zn} (\text{zener breakdown voltage}) = 7.6V$$

$$V_{BE} (\text{sat}) = 0.8V$$

$$V_{CE} (\text{sat}) = 0.2V$$

$$V_{BE} (\text{F.A}) = 0.7V$$

$$\text{Common emitter current gain, } \beta = 30$$

① One input low,

$$\text{So, } V_P = 0.8 + V_N$$

~~Malfunction occurs when  $D_1, D_2, T$  are~~


Malfunction occurs when  $Q_1, Q_2, D_3$  gets turned ON.

~~Orig~~; Originally the components,

$Q_1, Q_2, D_3$  are turned off because

The voltage is not enough to turn them on. When a minimum noise voltage is added, it might turn on the  $Q_1, Q_2, D_3$  components.

Now,

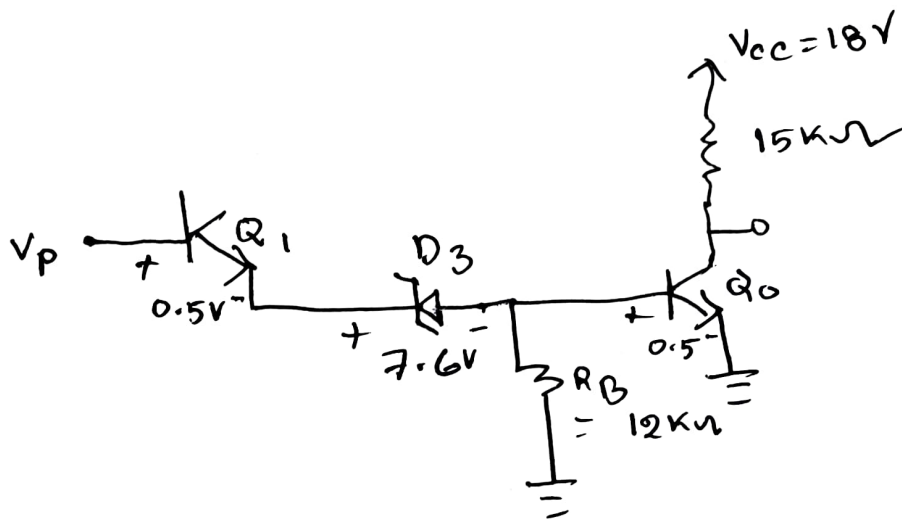

So,

$$V_P = 0.5 + 0.5 + 7.6$$

$$= 8.6$$

$$V_P = 0.8 + V_N$$

$$\Rightarrow 8.6 = 0.8 + V_N$$

$$\Rightarrow V_N = 7.8 \text{ V}$$


So, Low noise margin  $= V_N = 7.8V$

$$V_{NL} = 7.8V$$

(Ans)

(b)

if both inputs are high,  
then,

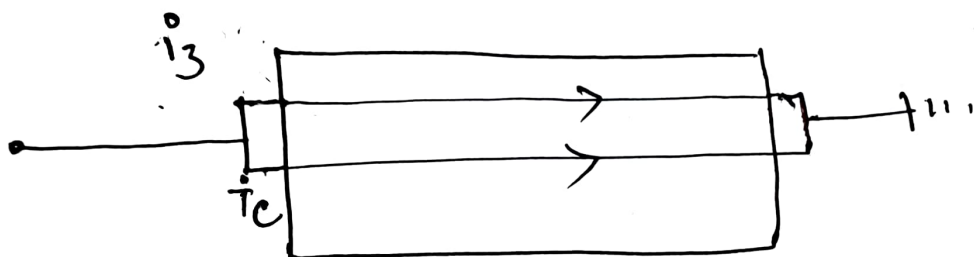

$$i_3 + i_2 = i_1$$

$$\Rightarrow i_3 = i_1 - i_2$$

$$i_3 = \beta I_{B1}$$

$$i_3 = \frac{\beta}{1+\beta} I_{E1}$$

$$\Rightarrow \beta I_{B1} = \frac{\beta}{1+\beta} I_{E1}$$

$$i_c = \frac{18 - 0.7}{15}$$

$$= 1.19 \text{ mA}$$

$$I_1 = \frac{18 - V_{e1}}{4}$$

$$I_E = (\beta + 1) I_B$$

$$\Rightarrow I_{E1} = (\beta + 1) I_2$$

$$\Rightarrow I_1 = (\beta + 1) I_2$$

$$\Rightarrow \frac{18 - V_{e1}}{4} = (30 + 1) \frac{V_{e1} - 9.1}{6}$$

$$\Rightarrow V_{e1} = 9.511 \text{ V}$$

$$I_2 = \frac{V_{e1} - 9.1}{R_2}$$

$$= \frac{V_{e1} - 9.1}{6}$$

$$= \frac{9.511 - 9.1}{6}$$

$$= 0.085 \text{ mA}$$

$$I_1 = \frac{18 - 9.511 \text{ V}}{4}$$

$$= 2.122 \text{ mA}$$

$$\text{So, Power dissipation} = (18 - 0) (2.122 + 1.19)$$

$$= 59.62 \text{ mW}$$

(ii)

$$i_c = 1.19 \text{ mA}$$

$$i_n = \frac{0.8}{12} = 0.067 \text{ mA}$$

$$i_B = i_{E1} - i_n$$

$$= 2.055 \text{ mA}$$

$$\beta_{min} = \frac{i_c}{i_B} = \frac{1.19}{2.055}$$

$$= 0.58 \text{ (minimum value)}$$

(Ans)