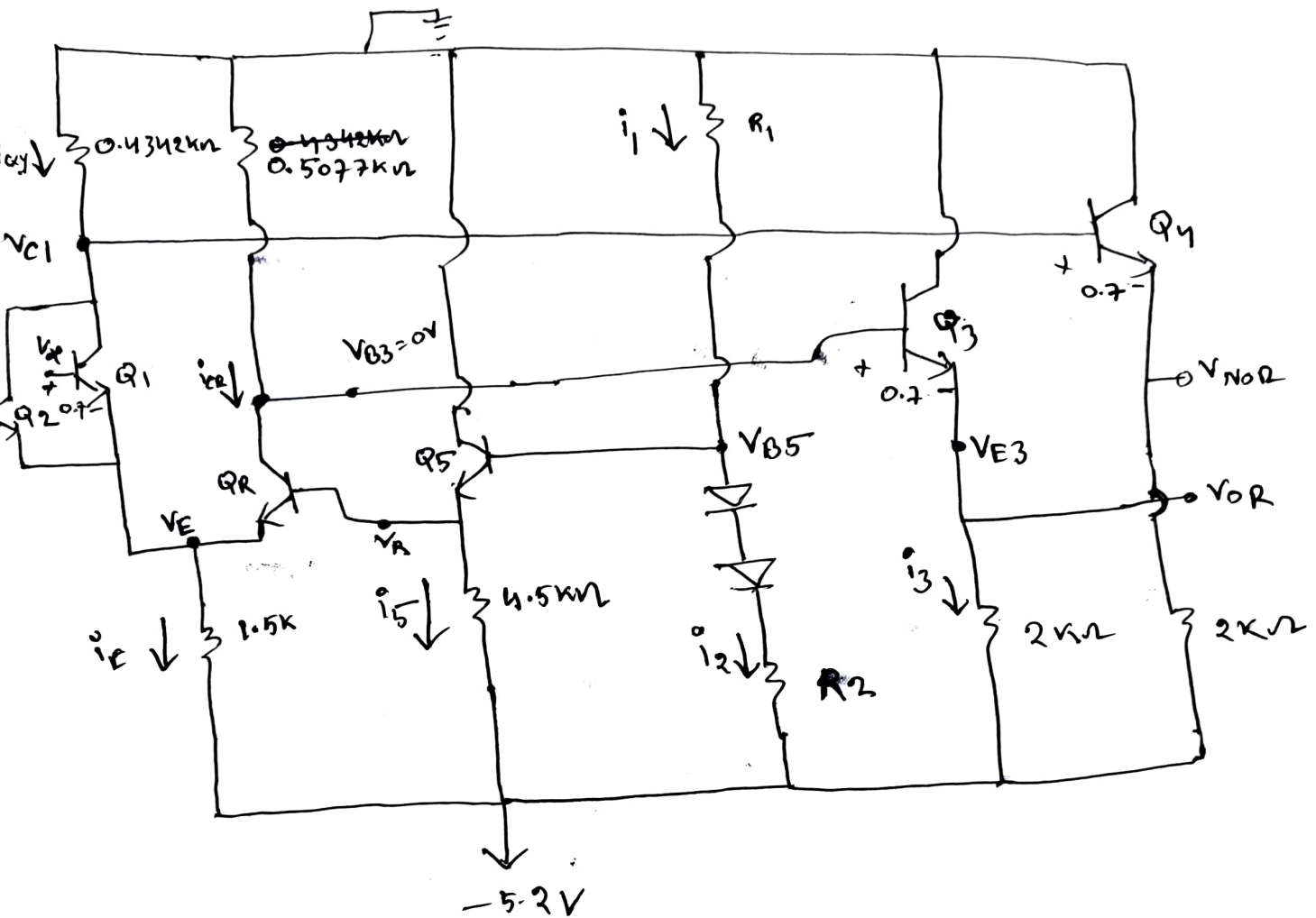


Name: Kazi Md. Al-Wakil

ID: 19301051

Sec: 12

Quiz: 3



(a) $V_x, V_y \rightarrow$ logical high

then, Q_1, Q_2 would turn on. In forward active mode.

Now,

Q_R in cut off

$$i_{CR} = 0 \text{ mA},$$

Q_3, Q_4 is in Forward active mode

So,

$$V_{B3} - V_{E3} = 0.7$$

$$\Rightarrow V_{E3} = 0 - 0.7$$

$$\Rightarrow V_{E3} = -0.7 \text{ V} = V_{OR}$$

As, V_x, V_y is in logical high,

$V_{OR} =$ logical high

$$= -0.7$$

logical high voltage = -0.7 V .

* Now, putting logical high = -0.7 V in the circuit

$$V_{x2} = V_y = -0.7 \text{ V}$$


$Q_1, Q_2 \rightarrow$ Forward active

Now,

$$V_{x2} - V_E = 0.7$$

$$\Rightarrow V_E = -0.7 - 0.7$$

$$\Rightarrow V_E = -1.4 \text{ V}$$

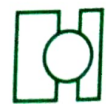

$$\text{So, } i_E = \frac{-1.4 - (-5.2)}{1.5k} = 2.53 \text{ mA}$$

As, $Q_R \rightarrow$ cut off

$$i_{CR} = 0 \text{ mA}$$

$$\text{So, } i_E = i_{cx} = 2.53 \text{ mA}$$

$$\text{So, } i_{cx} = \frac{0 - V_{C1}}{0.4342}$$

$$\Rightarrow 2.53 \times 0.4342 = -V_{C1}$$

$$\Rightarrow V_{C1} = -1.098526 \text{ V}$$

Now,

$$V_{C1} = V_{B4} = -1.098526$$

~~V_{NOR}~~

$$V_{B4} - V_{NOR} = 0.7$$

$$\Rightarrow V_{NOR} = V_{B4} - 0.7$$

$$\Rightarrow V_{NOR} = -1.098526 - 0.7$$

$$= -1.798526 \text{ [logical low]}$$

(Ans)

(b)

$$i_1 = i_2 = i_5$$

$$V_R = \frac{-0.7 - 1.798526}{2}$$

$$= -1.249 \text{ V}$$

$$i_5 = \frac{-1.249 + 5.2}{4.5 \text{ K}}$$

$$= \boxed{0.878 \text{ mA}}$$

$$V_{05} = -0.549$$

$$\text{So, } i_2 = \frac{-0.549 - 1.4 + 5.2}{R_2}$$

$$\Rightarrow \boxed{R_2 = 3.703 \text{ k}\Omega}$$

$$R_i = \frac{0 + 0.549}{0.878}$$

$$= \boxed{0.625 \text{ kW}} \quad \text{Ans)$$