



*Digital to Analog Converter*


# ADC and DAC 2

---


## LECTURE 14

This document might contain some excerpts and pictures from various books and other sources. The author doesn't claim any rights to the topics discussed in this video. This topics has been presented in a way to help out students in BRAC university, Bangladesh

# D/A Converter Operation

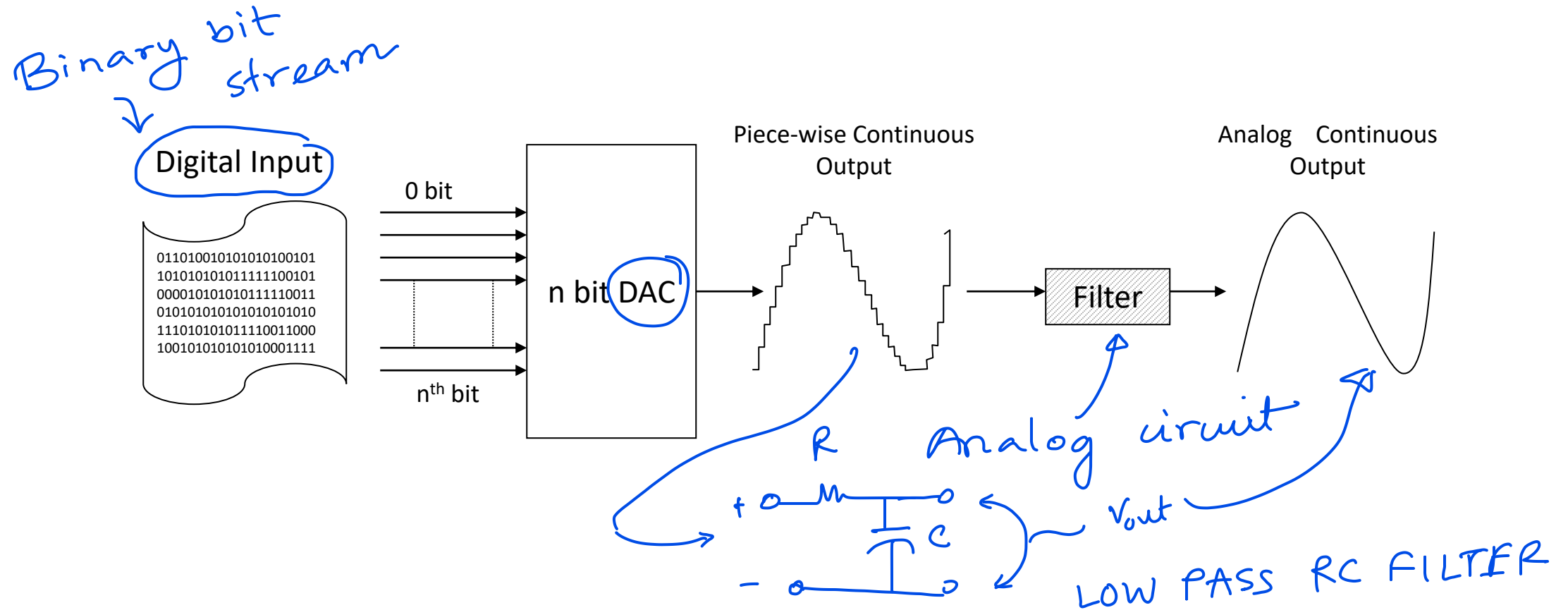

# Binary Weighted Resistor

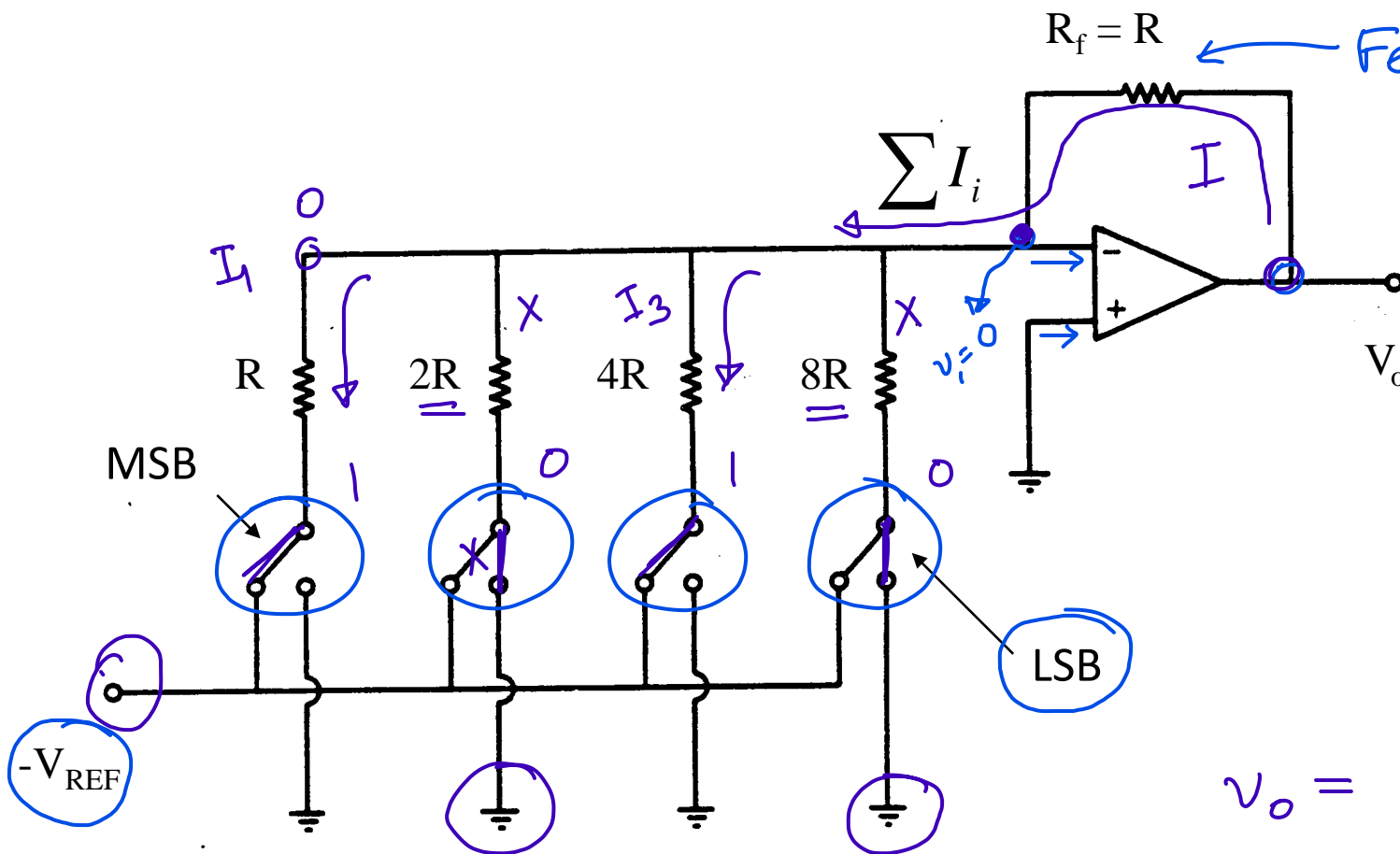

$$I = \frac{V_o - 0}{R} = \frac{V_o}{R}$$

$$I = I_1 + I_3$$


$$I_1 = \frac{0 - (-V_{REF})}{R} = \frac{V_{REF}}{R}$$

$$I_3 = \frac{V_{REF}}{4R}$$

1010

$$V_o = V_{REF} \times \left( \frac{1}{4} + 1 \right)$$

# Binary Weighted Resistor

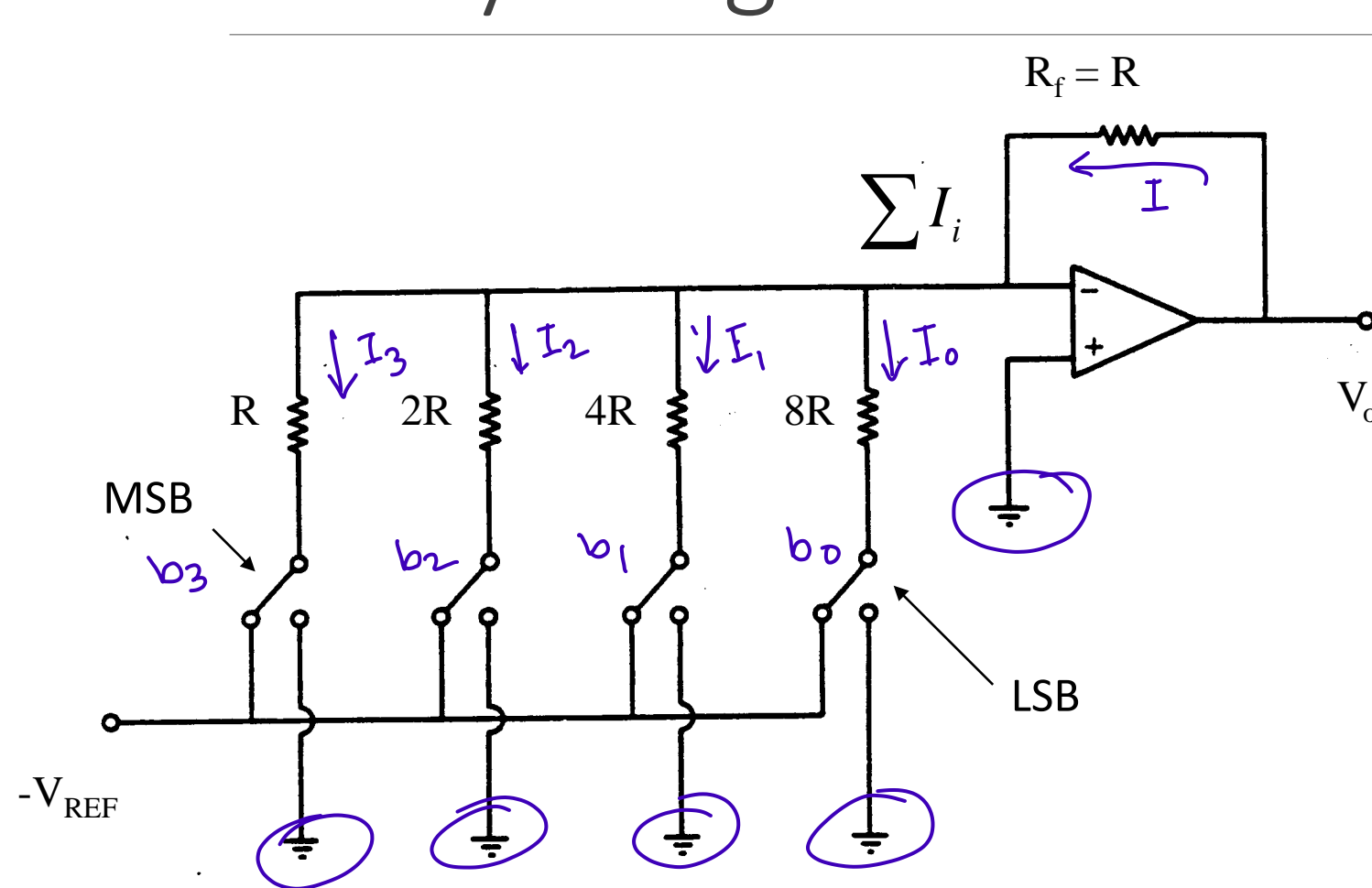



$$I_2 = b_2 \times \left( \frac{V_{REF}}{2R} \right)$$

$$I = I_1 + I_2 + I_3 + I_0$$

$$\Rightarrow V_o = V_{REF} \left( b_3 + \frac{b_2}{2} + \frac{b_1}{4} + \frac{b_0}{8} \right)$$

# R-2R Ladder

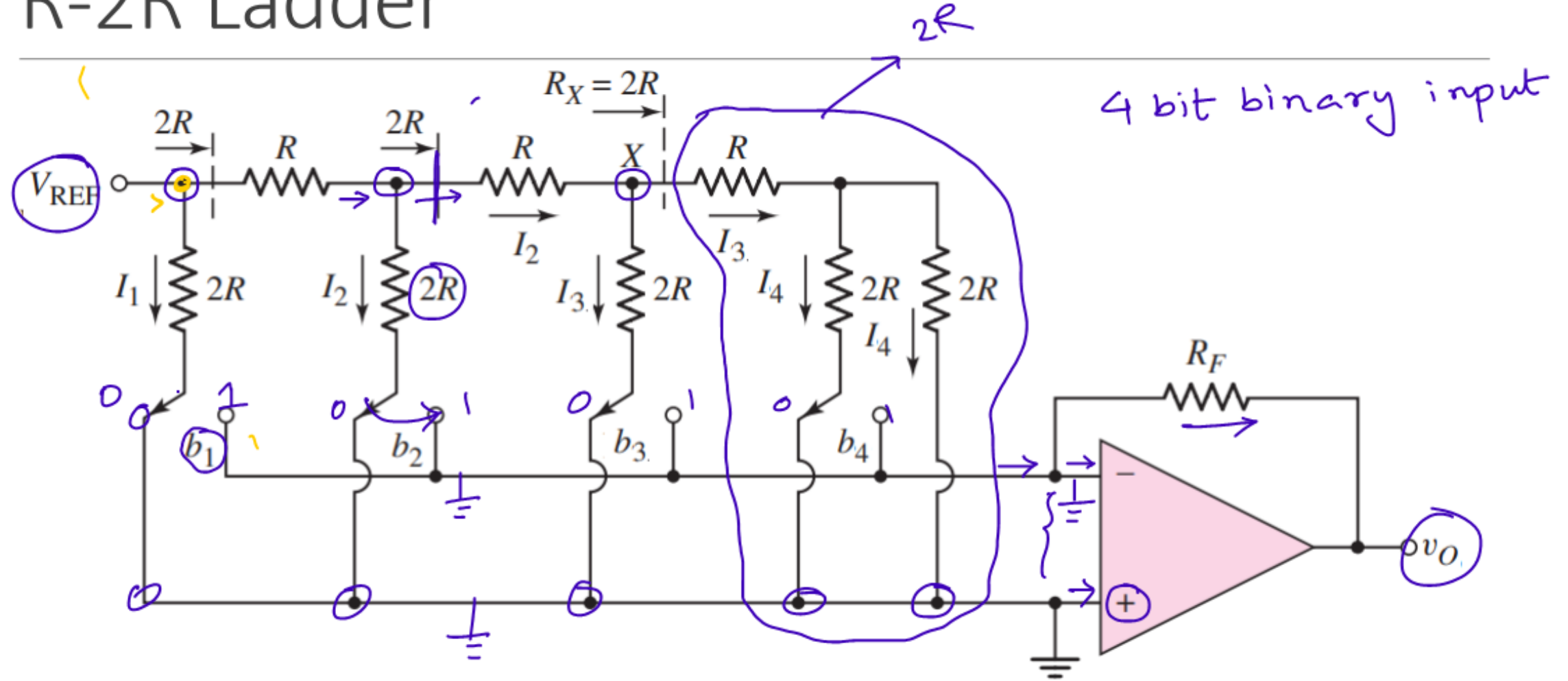

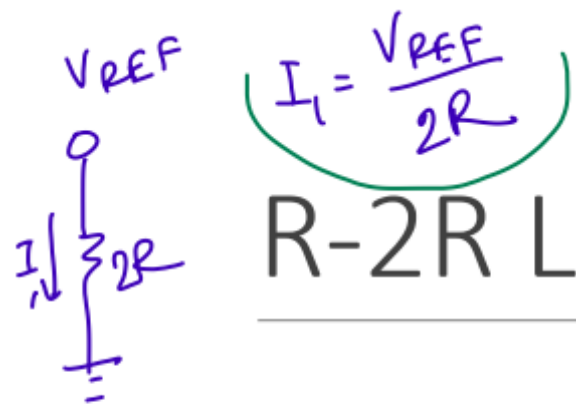

Handwritten equation:  $I_1 = \frac{V_{REF}}{2R}$

# R-2R Ladder


Handwritten equations:  $I'_1 = b_1 I_1$ ,  $I'_2 = b_2 I_2$ ,  $I'_3 = b_3 I_3$ ,  $I'_4 = b_4 I_4$

Handwritten equation:  $\bar{I} = I'_1 + I'_2 + I'_3 + I'_4$

Handwritten equation:  $= b_1 I_1 + b_2 I_2 + b_3 I_3 + b_4 I_4$


Handwritten equation:  $= b_1 I_1 + b_2 \frac{I_1}{2} + b_3 \frac{I_3}{4} + b_4 \frac{I_4}{8}$

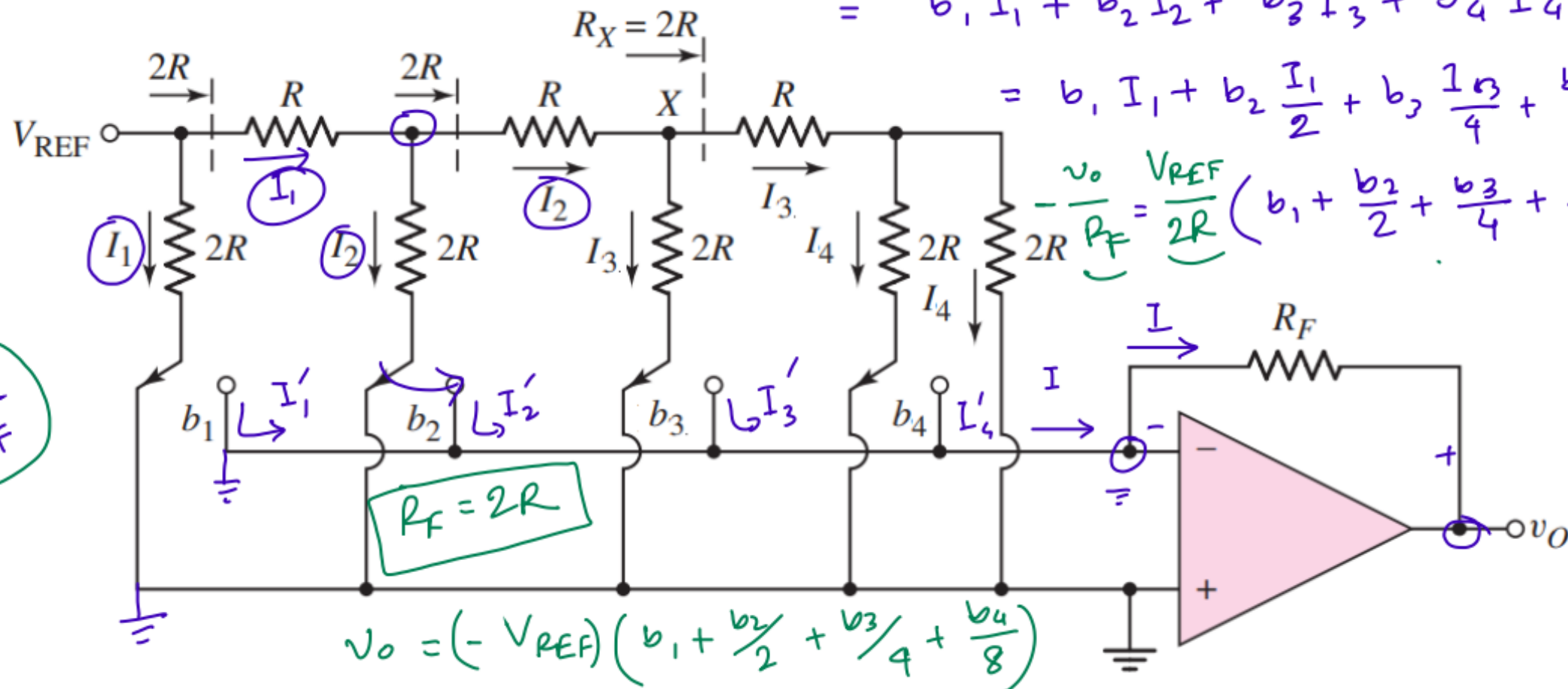Handwritten equation:  $-\frac{v_o}{R_F} = \frac{V_{REF}}{2R} \left( b_1 + \frac{b_2}{2} + \frac{b_3}{4} + \frac{b_4}{8} \right)$



Handwritten equation:  $v_O = (-V_{REF}) \left( b_1 + \frac{b_2}{2} + \frac{b_3}{4} + \frac{b_4}{8} \right)$

# Performance Specifications

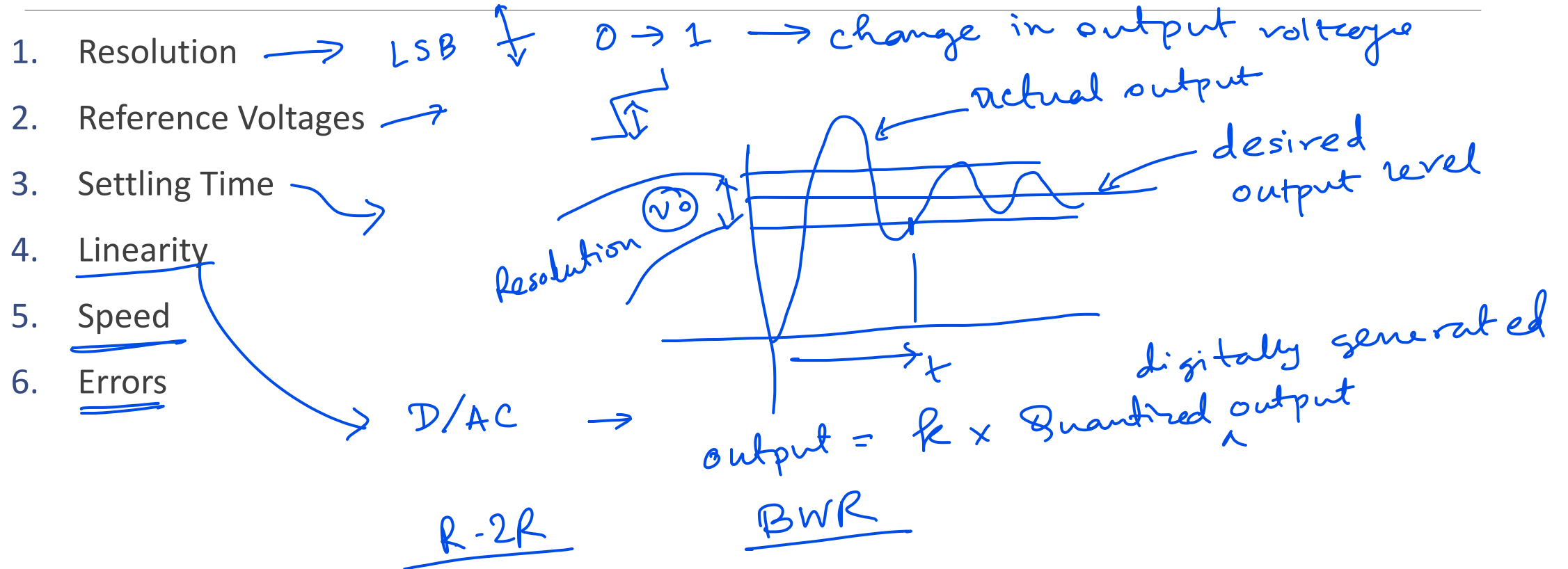


# Successive Approximation ADC

$\frac{S}{\Delta} \frac{A}{T} \underline{R} \leftarrow \text{Register}$   
 $\underline{S} \underline{R} \underline{G}$   
 Shift Register Generator
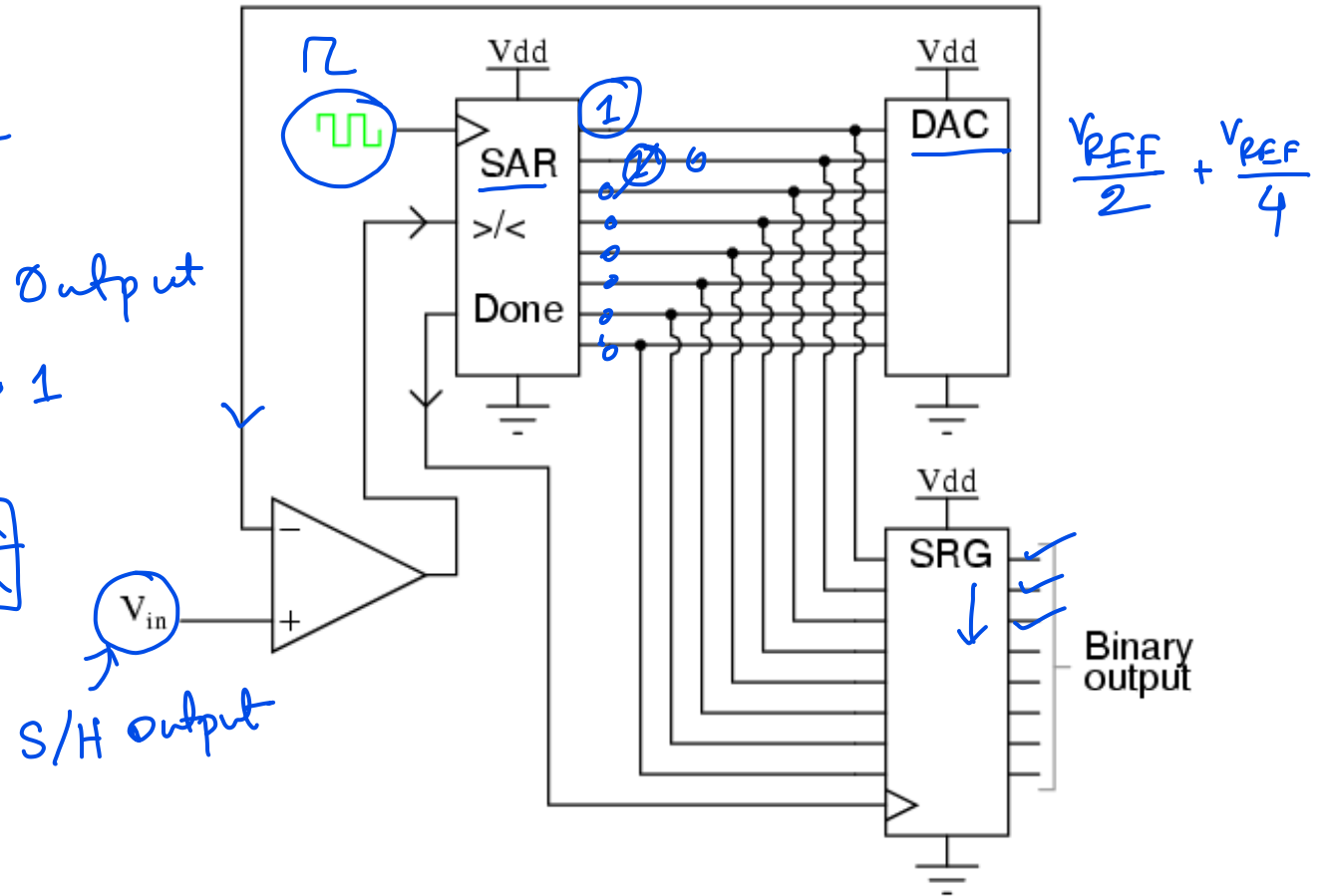
# Binary Search

- ① S/H output is applied to the  $V_{in}$  at  $t = 0$ .
- ② Next pulse will reset Binary Output
- ③ if  $V_{in} > \frac{V_{REF}}{2}$ , set the MSB  $\rightarrow 1$
- ④ if  $V_{in} > \left( \frac{0}{2} + \frac{V_{REF}}{4} \right)$  set  $\begin{matrix} 1 \\ 0 \end{matrix} \begin{matrix} \times \\ \times \end{matrix}$





# Example SAR

- 10 bit resolution or 0.0009765625V of Vref
- $V_{in} = .6$  volts
- $V_{ref} = 1$  volts
- Find the digital value of  $V_{in}$  →

\* binary 

1	0	0	0	0	0	0	0	0	0
---	---	---	---	---	---	---	---	---	---

 → DAC

$0.5 < 0.6$

\* binary  $1 \times 00000000 \xrightarrow{DAC} 0.5 + 0.25 = 0.75$   
 $0.6 < 0.75 \rightarrow SAR \rightarrow 1010000000$

\*  $0.5 + 0.125 \rightarrow 0.625 > 0.6$   
 $100100000000 \rightarrow 0.5 + 0.625 = 0.5625$   
 $0.6 > 0.5625 \rightarrow SAR \rightarrow 1001100000$

$\frac{1}{2} = 0.5$   
 ↑  
 DAC

Bit	Voltage
9	.5
8	.25
7	.125
6	.0625
5	.03125
4	<u>.015625</u>
3	<u>.0078125</u>
2	.00390625
1	.001953125
0	.0009765625

# Example

$$\begin{array}{r}
 1001100000 \rightarrow \text{DAC} \\
 * 0.5625 \\
 + 0.03125 \\
 \hline
 0.59375 < 0.6
 \end{array}$$


$$\begin{array}{r}
 1001100000 \rightarrow \text{DAC} \\
 0.59375 \\
 + 0.015625 \\
 \hline
 0.609375 > 0.6 \\
 \hline
 1001101000 \rightarrow \text{DAC} \\
 0.59375 \\
 + 0.0078125 \\
 \hline
 0.6015625 > 0.6 \\
 \hline
 1001100110
 \end{array}$$

•Digital Results:


1  
10bit

MSB	MSB-1	MSB-2	MSB-3	...					LSB
1	0	0	1	1	0	0	1	1	0

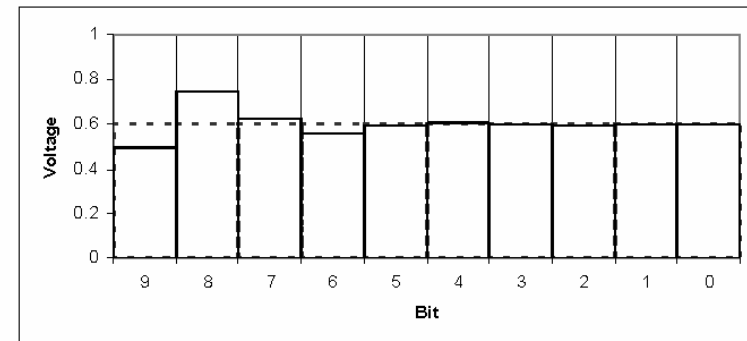
•Results:  $\frac{1}{2} + \frac{1}{16} + \frac{1}{32} + \frac{1}{256} + \frac{1}{512} = .599609375 \text{ V}$   $\rightarrow 0.6$



# Output

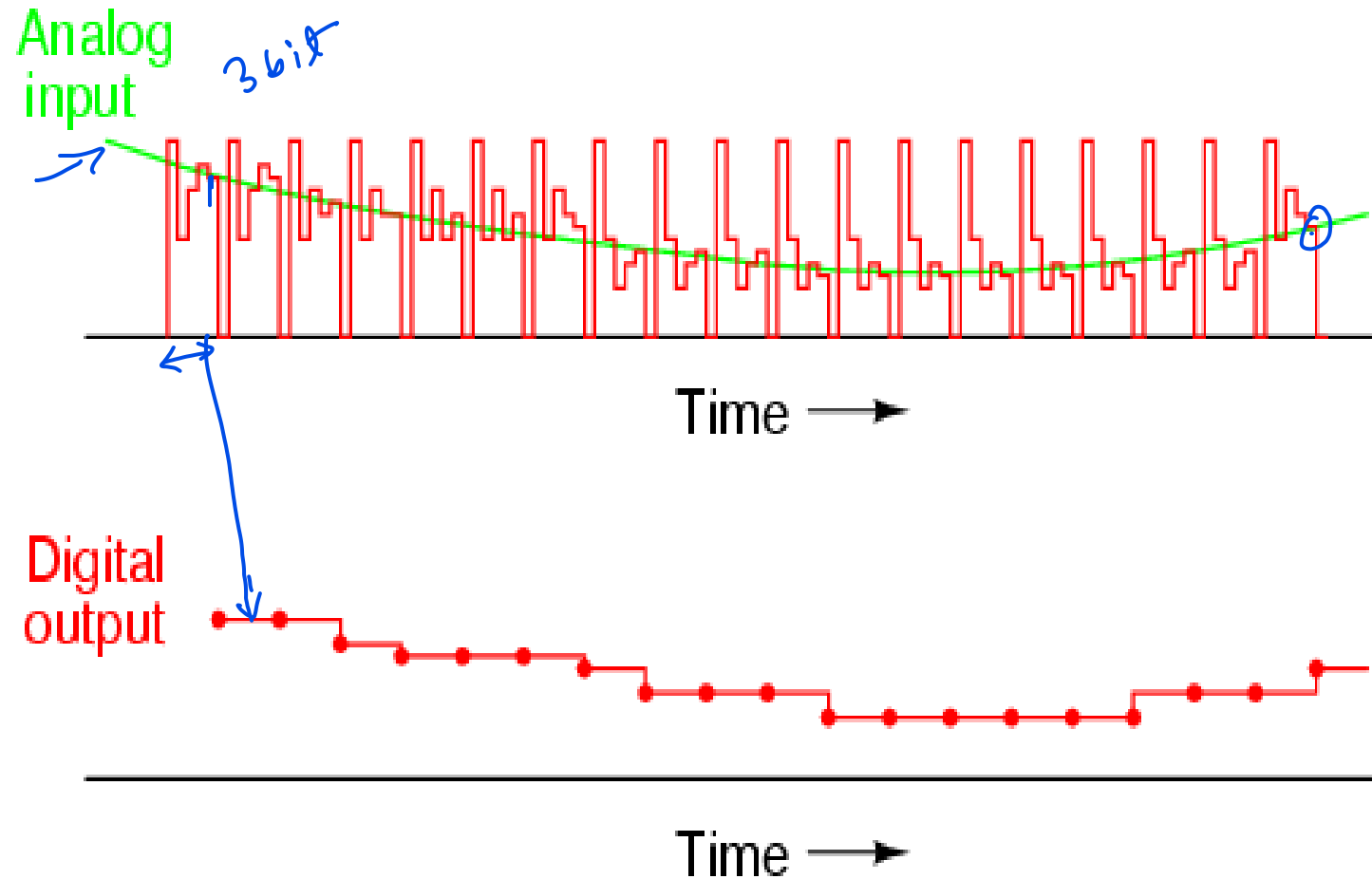

# A/D Converter Types Comparison

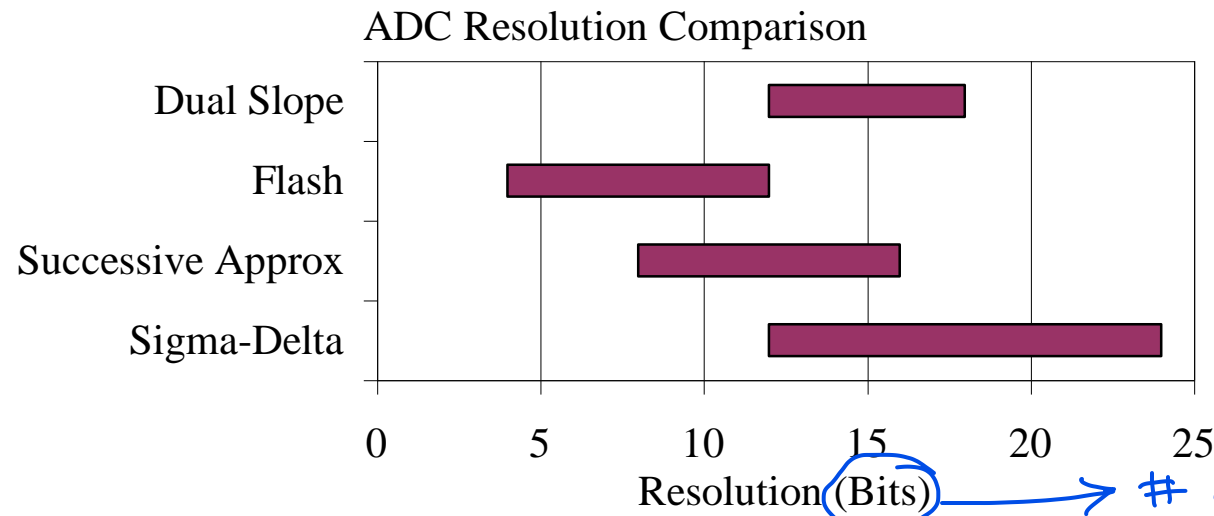

Type	Speed (relative)	Cost (relative)
Dual Slope →	Slow	Med
Flash	Very Fast	High
Successive Approx	Medium – Fast	Low
Sigma-Delta	Slow	Low

→ Accurate →  
→ 10 bit ADC.  $2^{10}, 2^{10}-1$

# Reference

---

- ❑ [https://ume.gatech.edu/mechatronics\\_course/ADC\\_F08.pdf](https://ume.gatech.edu/mechatronics_course/ADC_F08.pdf) ✓
- ❑ [http://ume.gatech.edu/mechatronics\\_course/DAC\\_S05.ppt](http://ume.gatech.edu/mechatronics_course/DAC_S05.ppt) ✓
- ❑ Chapter 16 of Electronic Circuits Analysis and Design by Donald A Neamen, 4<sup>th</sup> Edition
- ❑ [https://ebookbou.edu.bd/Books/Text/SST/DCSA/dcsa\\_2301/Unit-07.pdf](https://ebookbou.edu.bd/Books/Text/SST/DCSA/dcsa_2301/Unit-07.pdf) ✓